
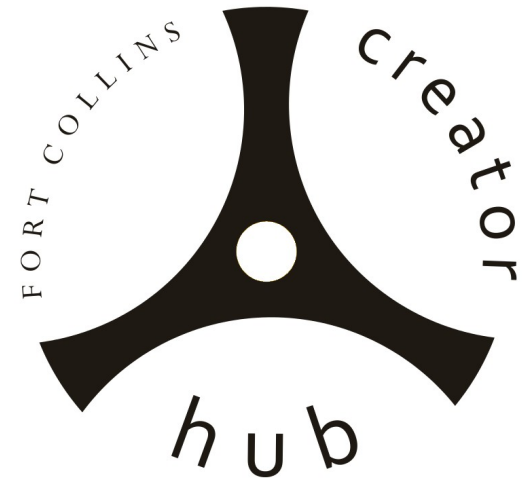


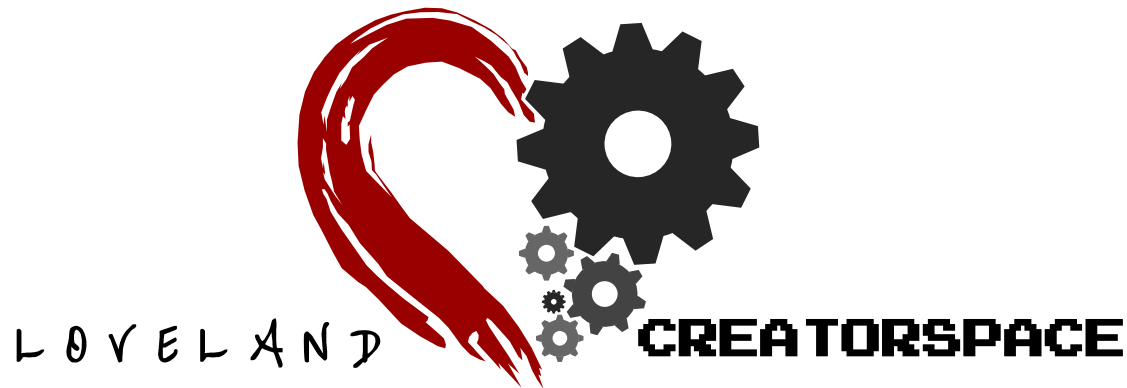Building Oscillating Circuits (multivibrators) Using Transistors




Introduction

- What is a multivibrator?
- Different types (bistable, monostable, bistable)
- Walk through of the circuits
- Build the circuits

What's a multivibrator?

- Circuit that has two states, and changes (vibrates, oscillates) between them
- Bistable – Stable in both states (Bi: 2)
 - Moves between states only when forced externally
- Monostable – Stable in just one state (Mono: 1)
 - Moves from state A to B by external force
 - Moves from state B to A after a time delay
- Astable – Stable in neither state (A: Not)
 - Autonomously oscillates between the states


LED Circuit

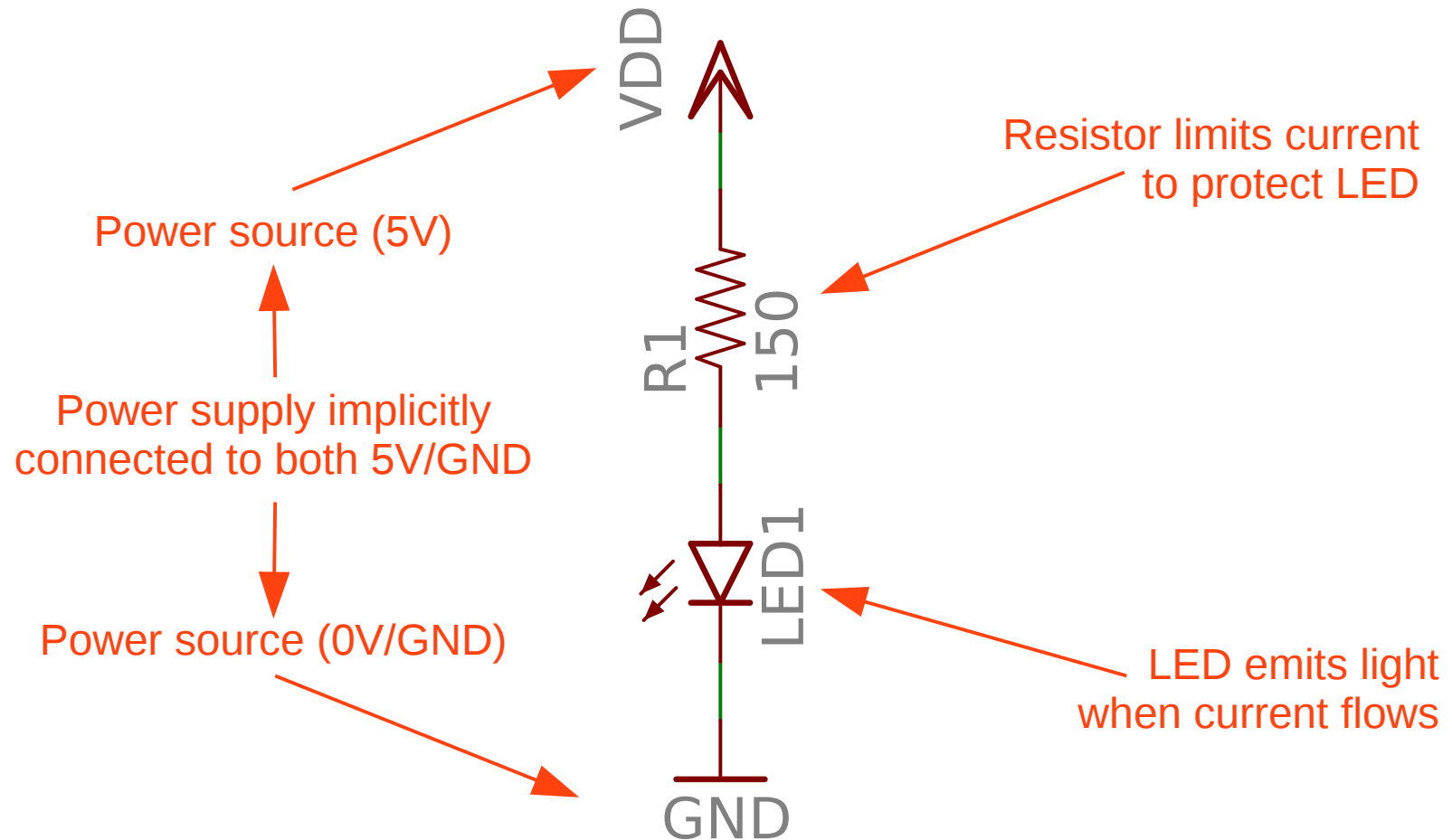


(Bipolar) Transistors

- A transistor can be a switch, or electronically controlled variable resistor
- Transistors generally have 3 pins
- For Bipolar transistors, these are named:
 - Collector
 - Base
 - Emitter
- Base voltage controls whether (how much) the Collector and Emitter are connected


Transistor – Pictures and Symbols

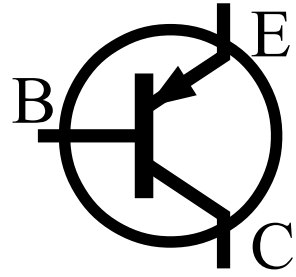

PNP
(**P**ointing **iN** **P**roudly)

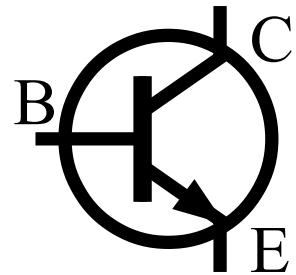


NPN
(**N**ot **P**ointing **iN**)

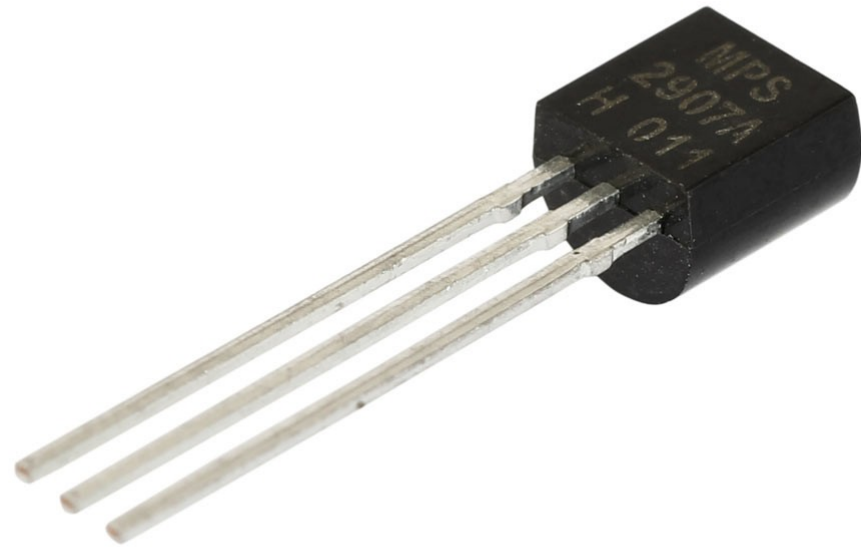


Transistors - Operation

- Base-Emitter current determines Collector-Emitter current
- Transistors often characterized as amplifying current:
The more Base current flows,
the more Collector-Emitter current can flow.
- A Base voltage is required
to cause a Base current to flow
- NPN: Turns on when Base is high (cf. Emitter)
- PNP: Turns on when Base is low (cf. Emitter)

Transistor Circuit

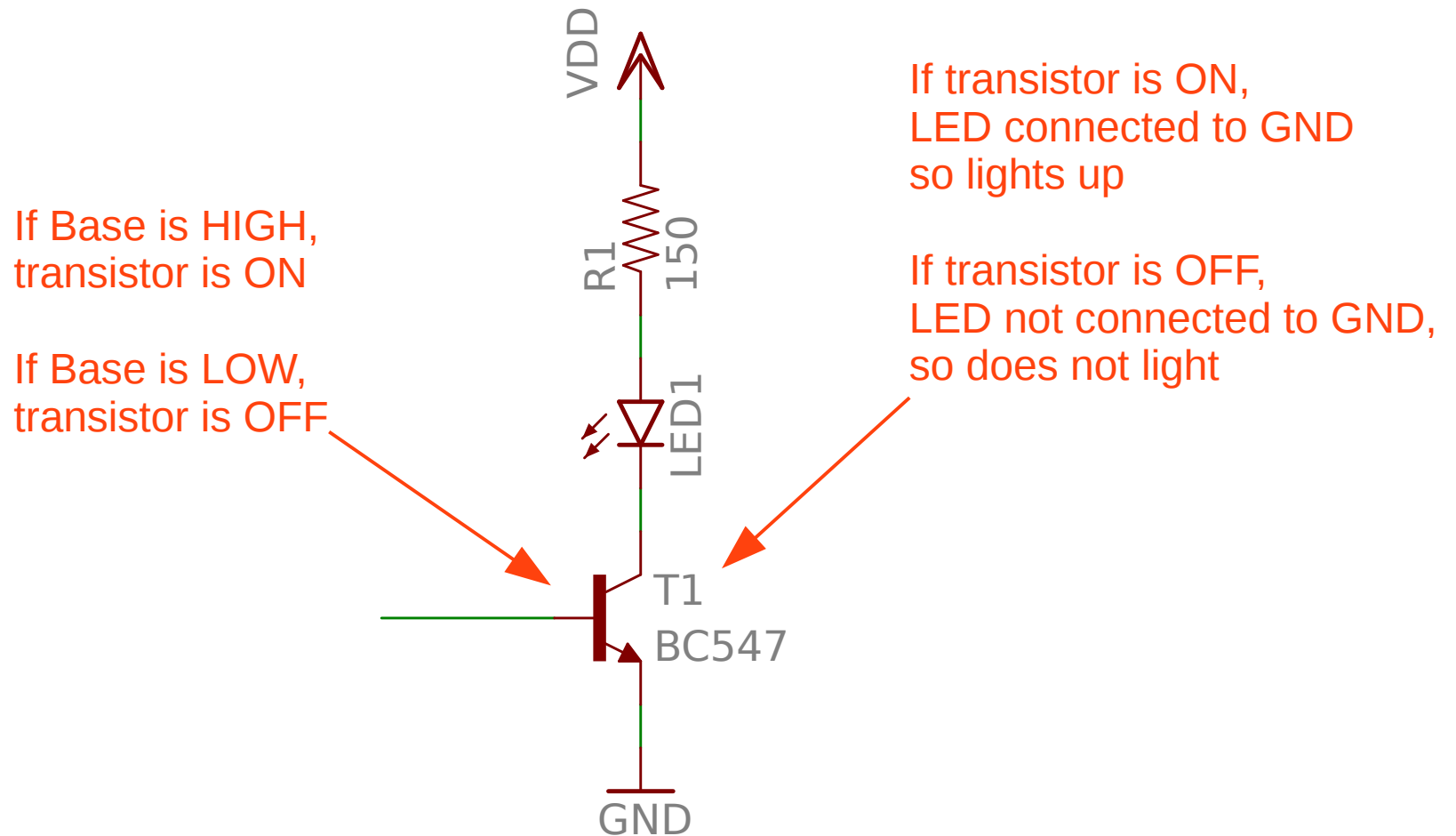


Bistable Circuit

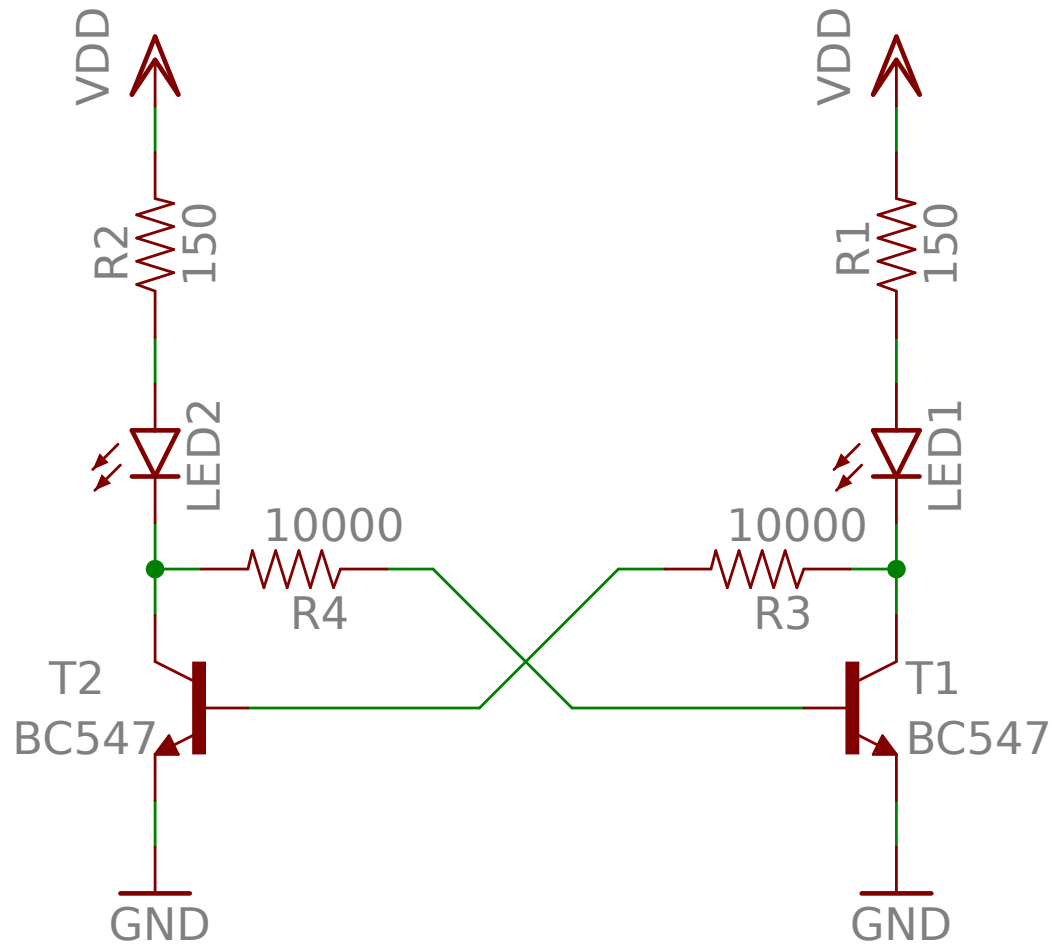


Bistable Circuit

Circuit from before

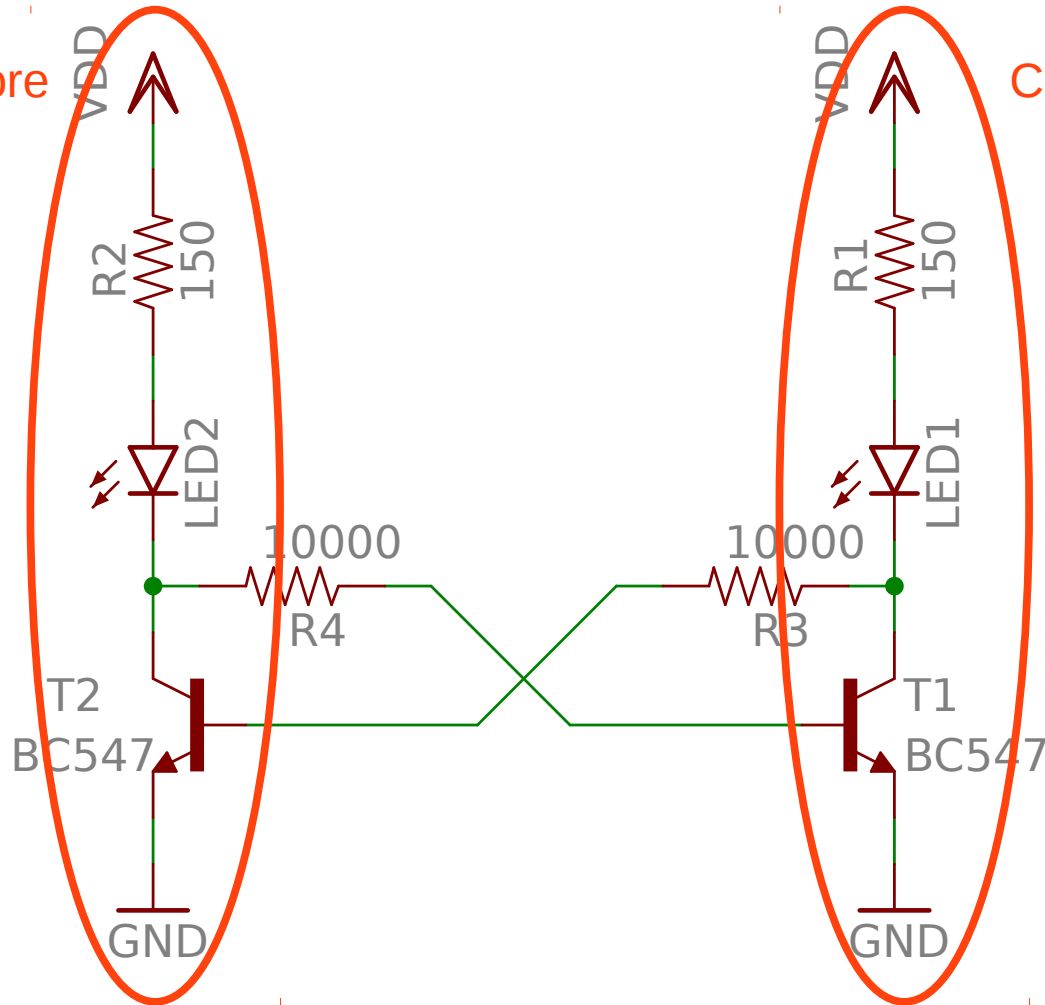


Circuit from before


Bistable Circuit

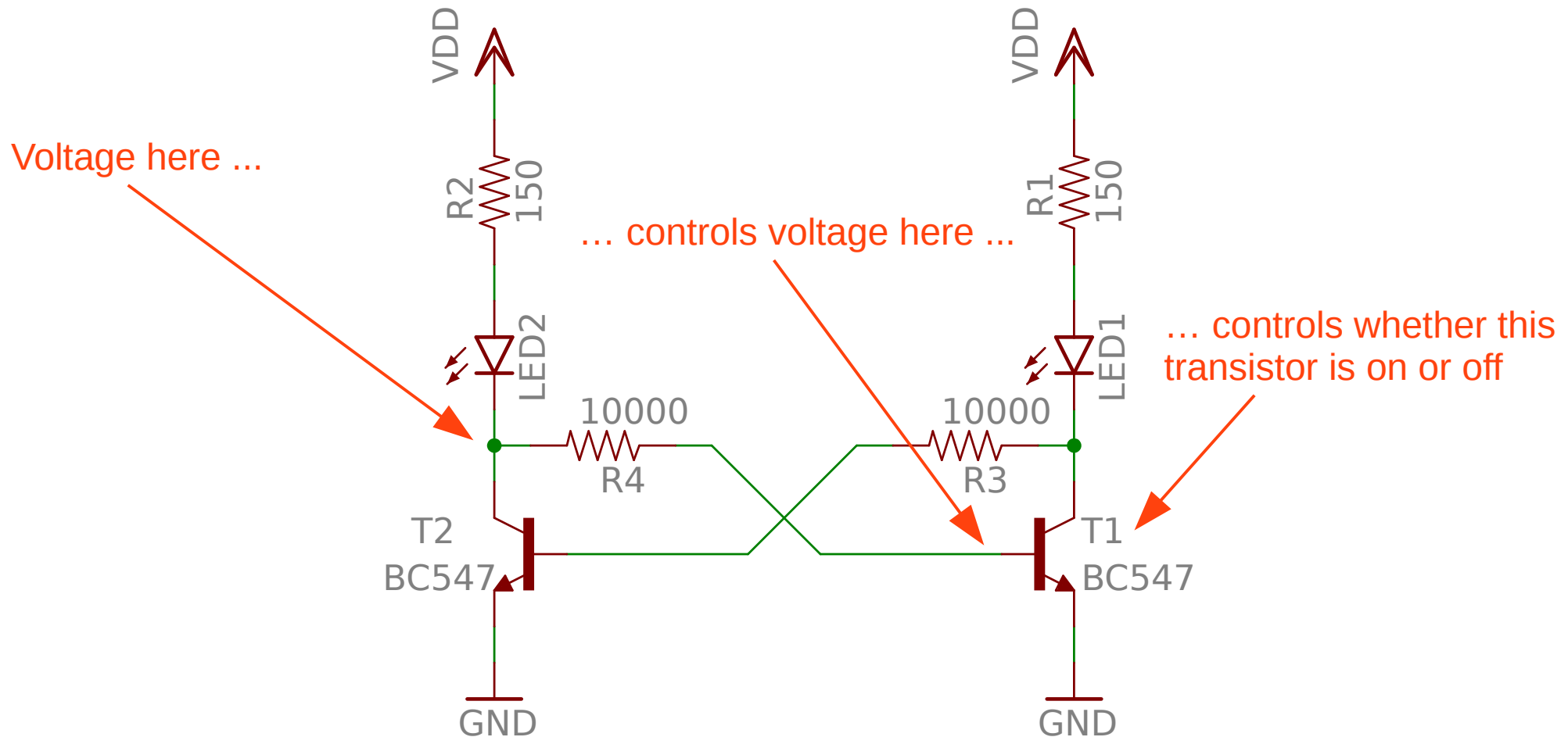


Bistable Circuit

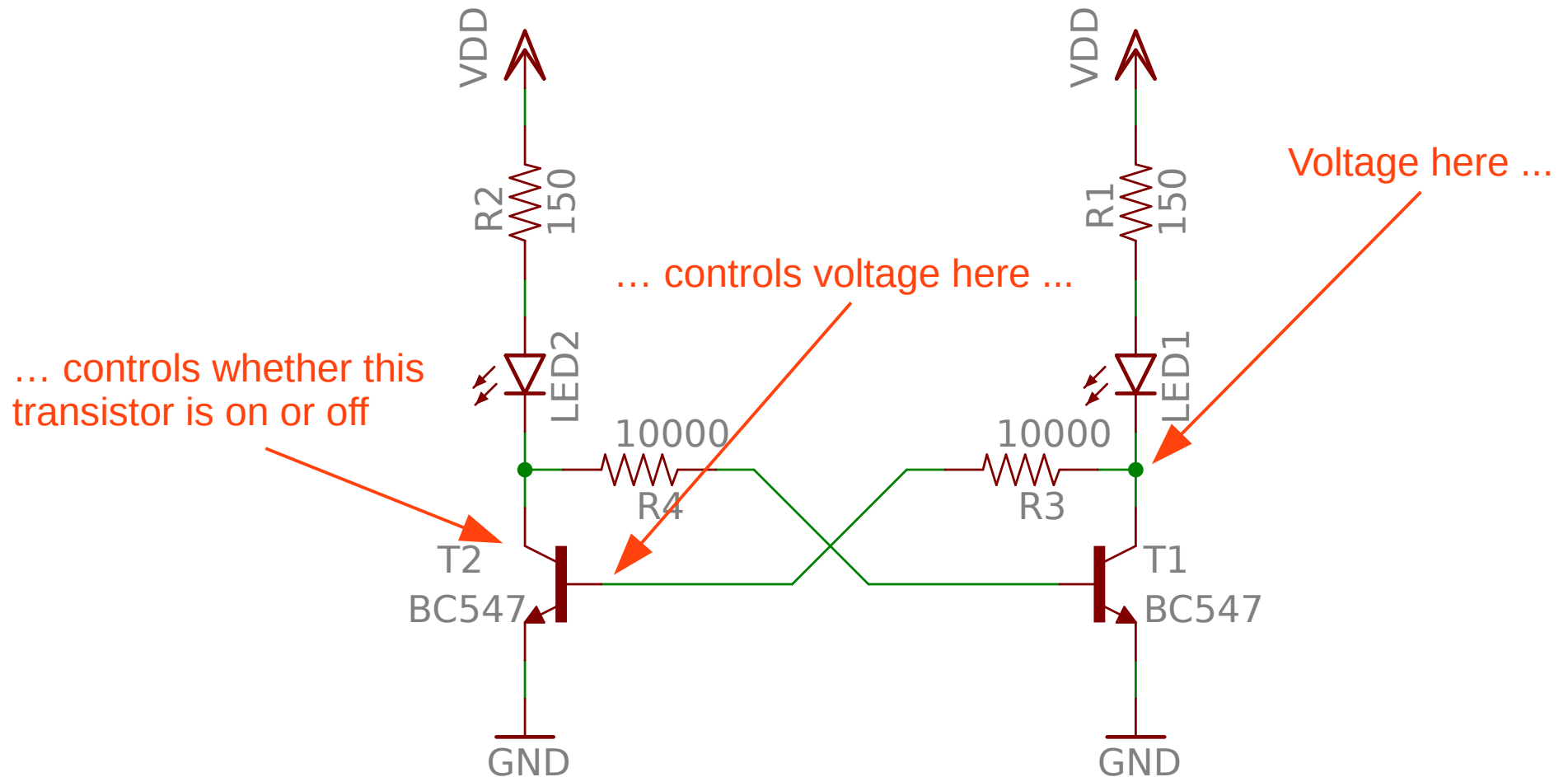


Bistable Circuit

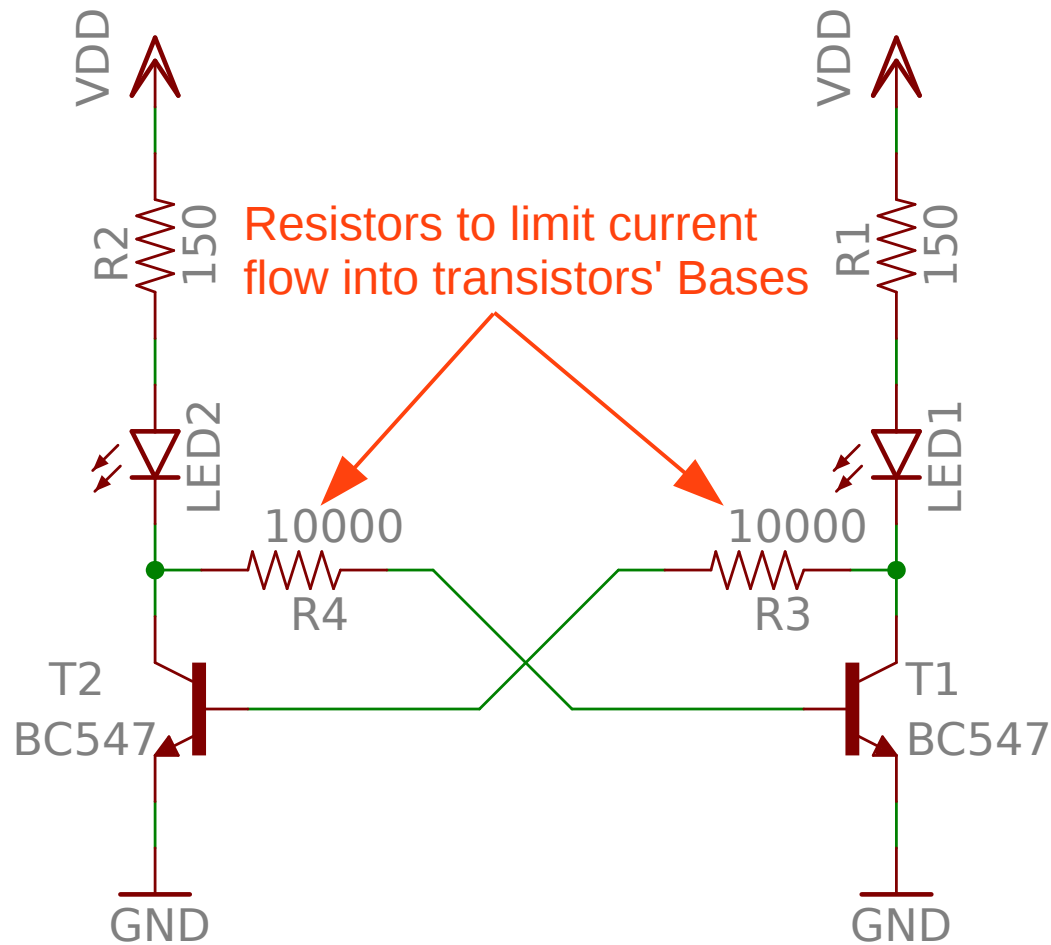


Bistable Circuit

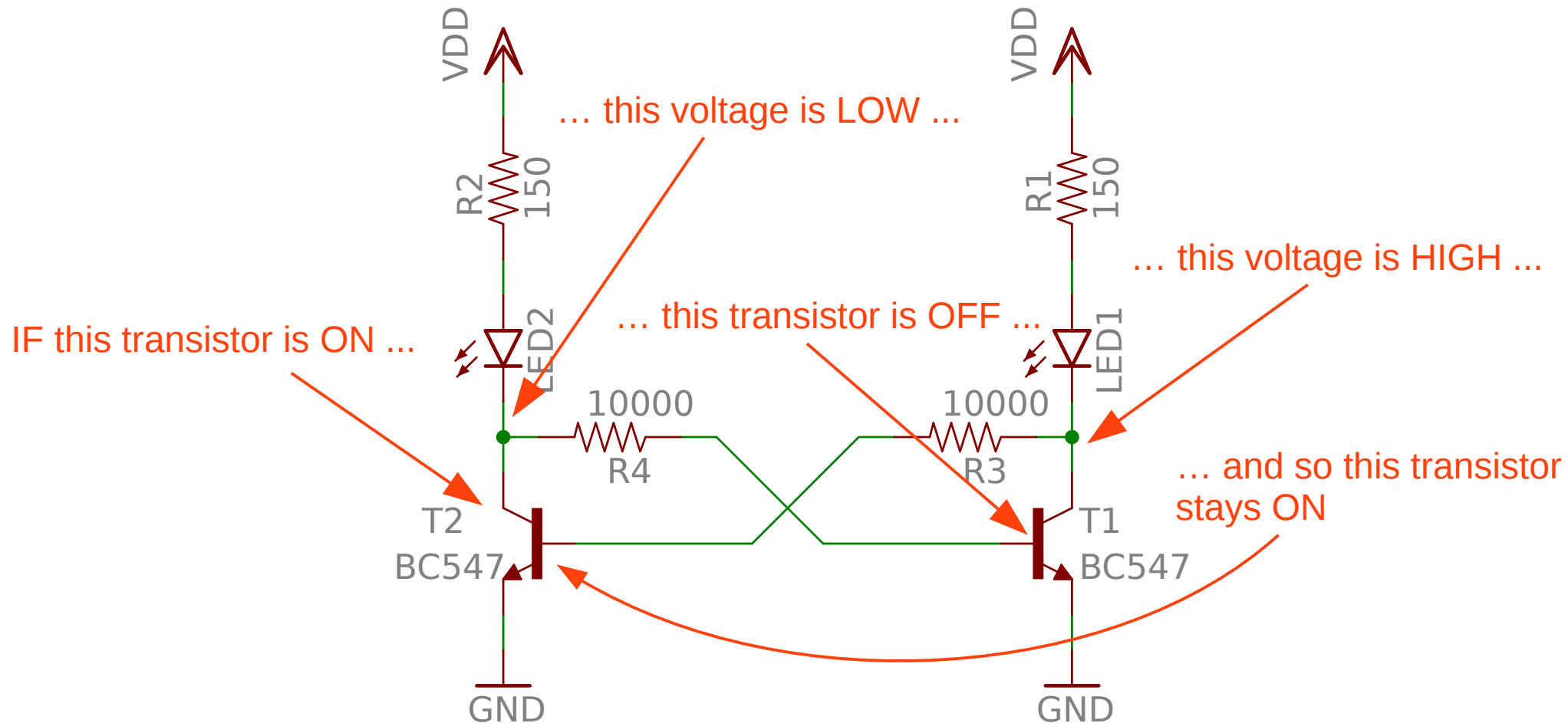

Bistable Circuit

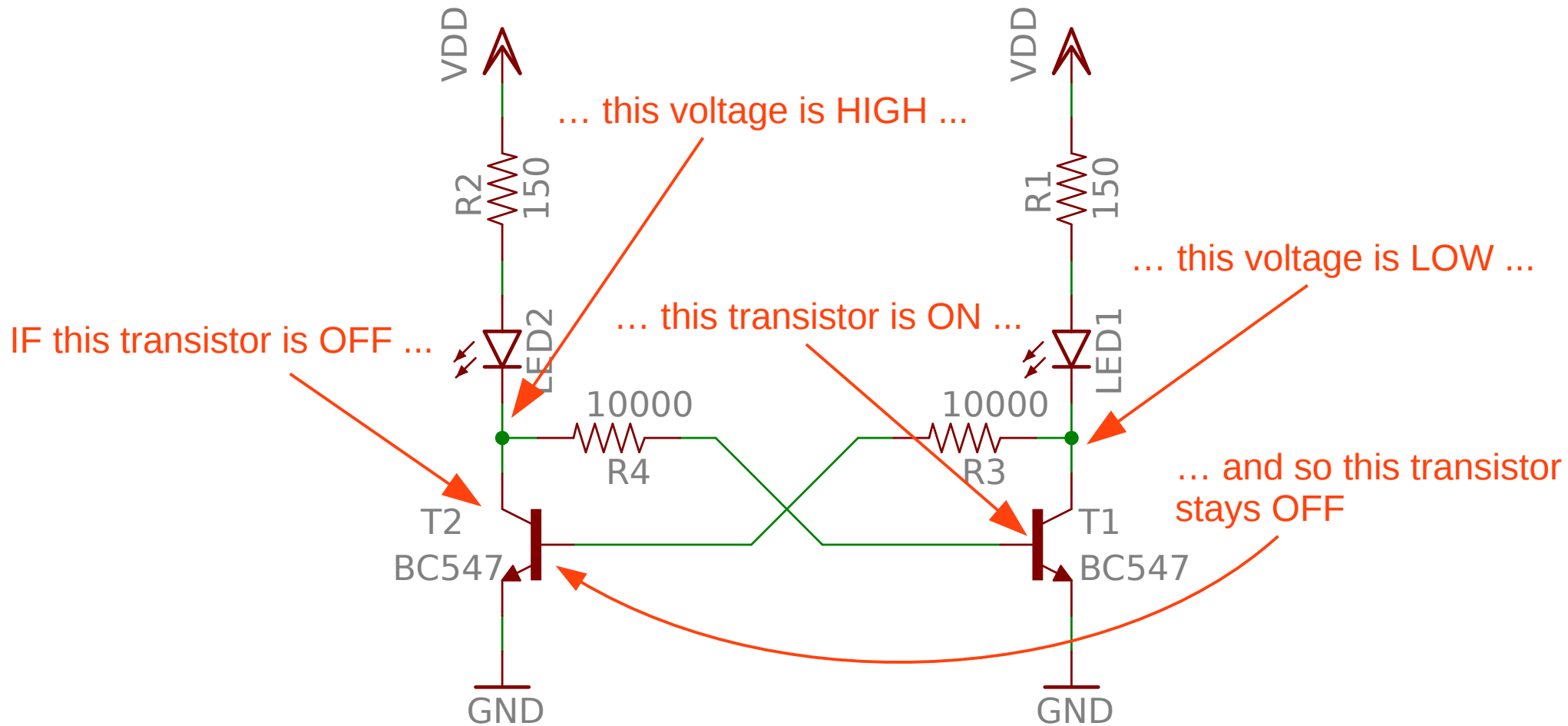

Bistable Circuit

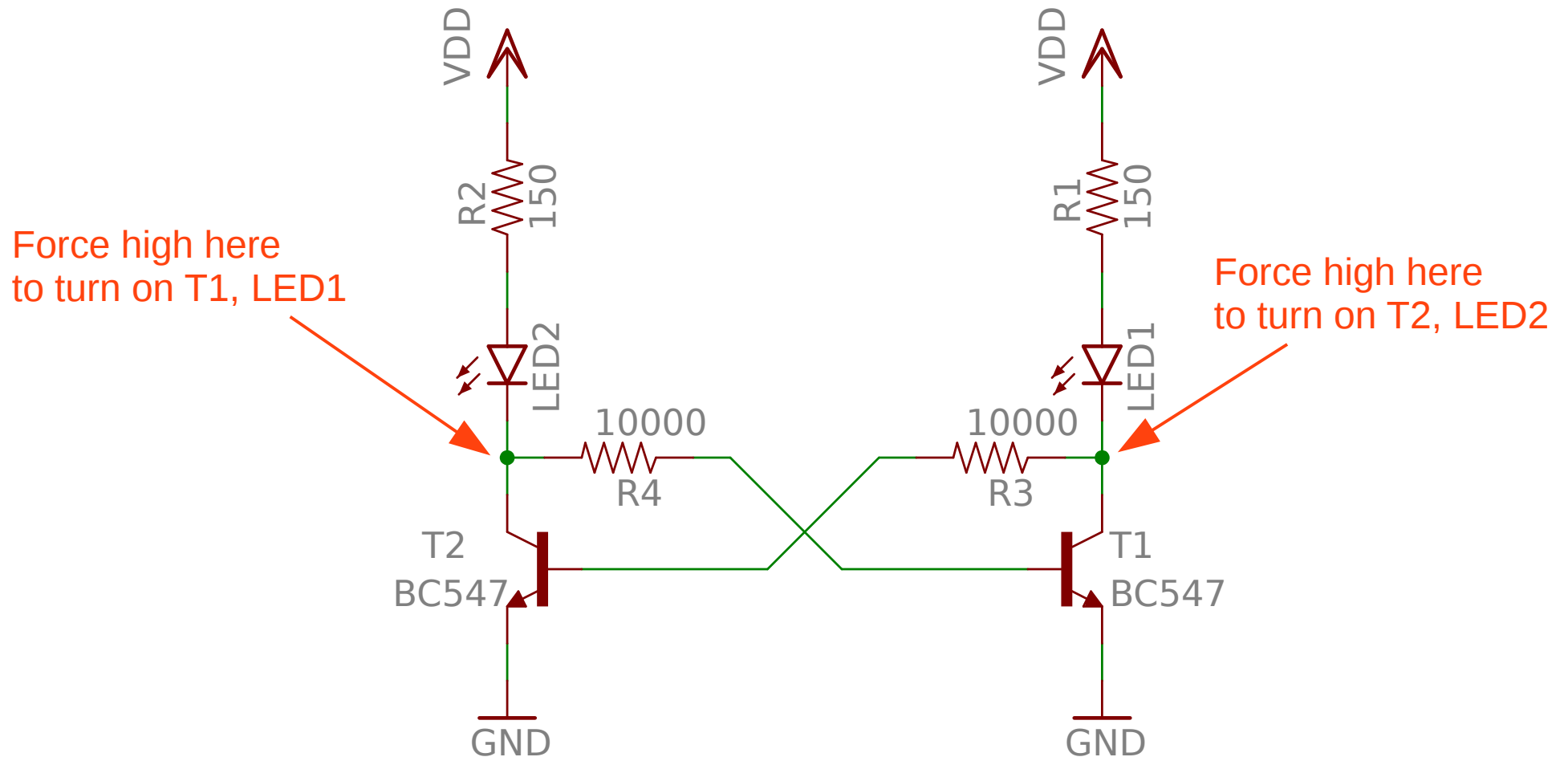

Bistable Animation

<http://www.falstad.com/circuit/e-multivib-bi.html>

Let's Build The Circuit!

Breadboards

- Used for quick circuit prototyping
- Holes to plug components' wires into
- Internal wires connect some of the holes

Rows are named


Columns are numbered

Gutter for ICs

Power rails along edges

Main body is columns of 5 connected holes


Two sides of gutter not connected

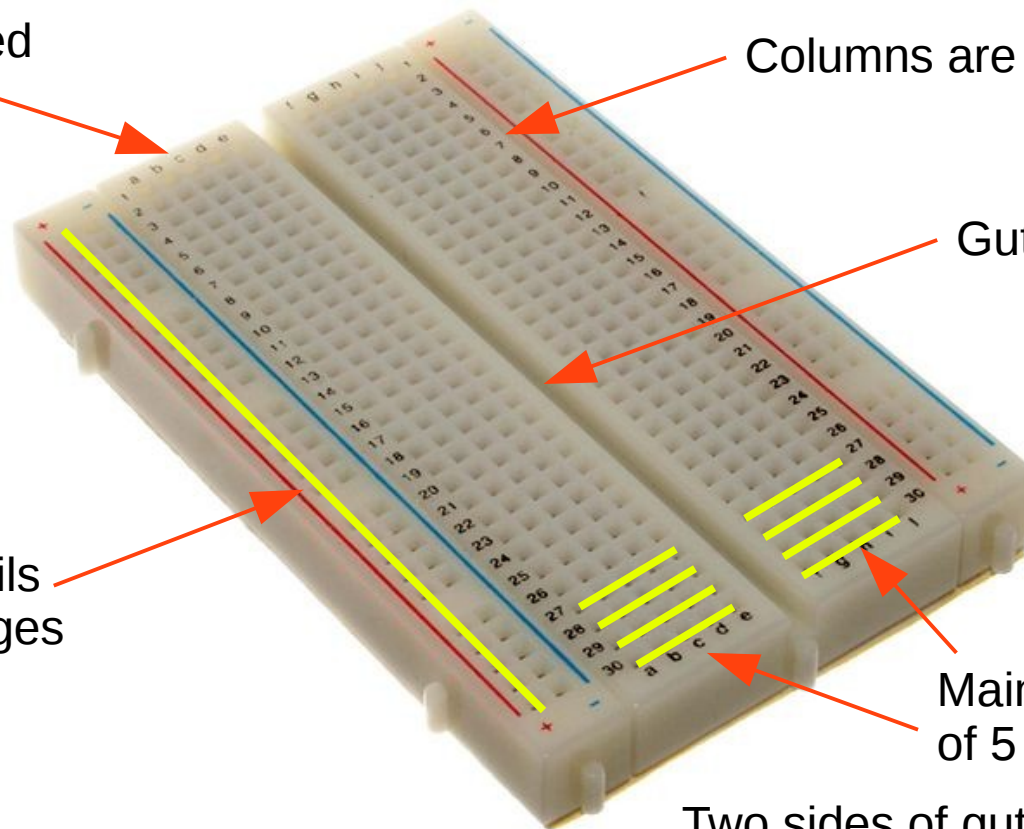

Placing components


- Polarity
 - Some components don't work backwards
- Don't bend pins
 - Slight angling OK, no need for kinks
- Don't burn out LEDs
 - By connecting to power with no resistor
- Don't connect power until circuit is complete

Transistor Packages

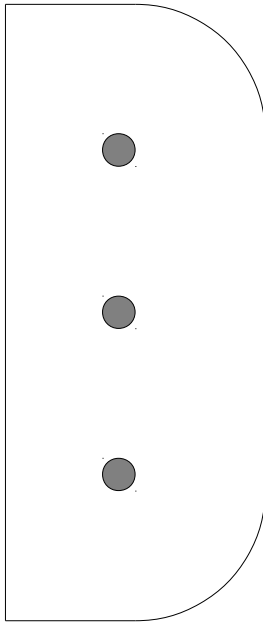

E-line package

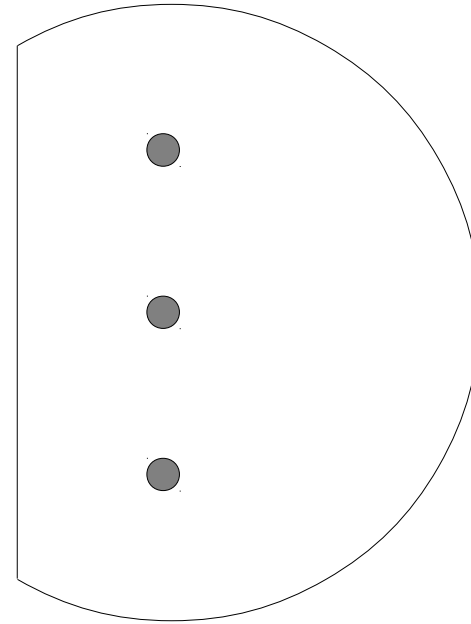
Kit contains:
ZVP2110A (we won't use this)




TO-92 package

Kit contains:
BC547 (use this; has pink dot on back)
BS170 (we won't use this)

Bistable – Step 1

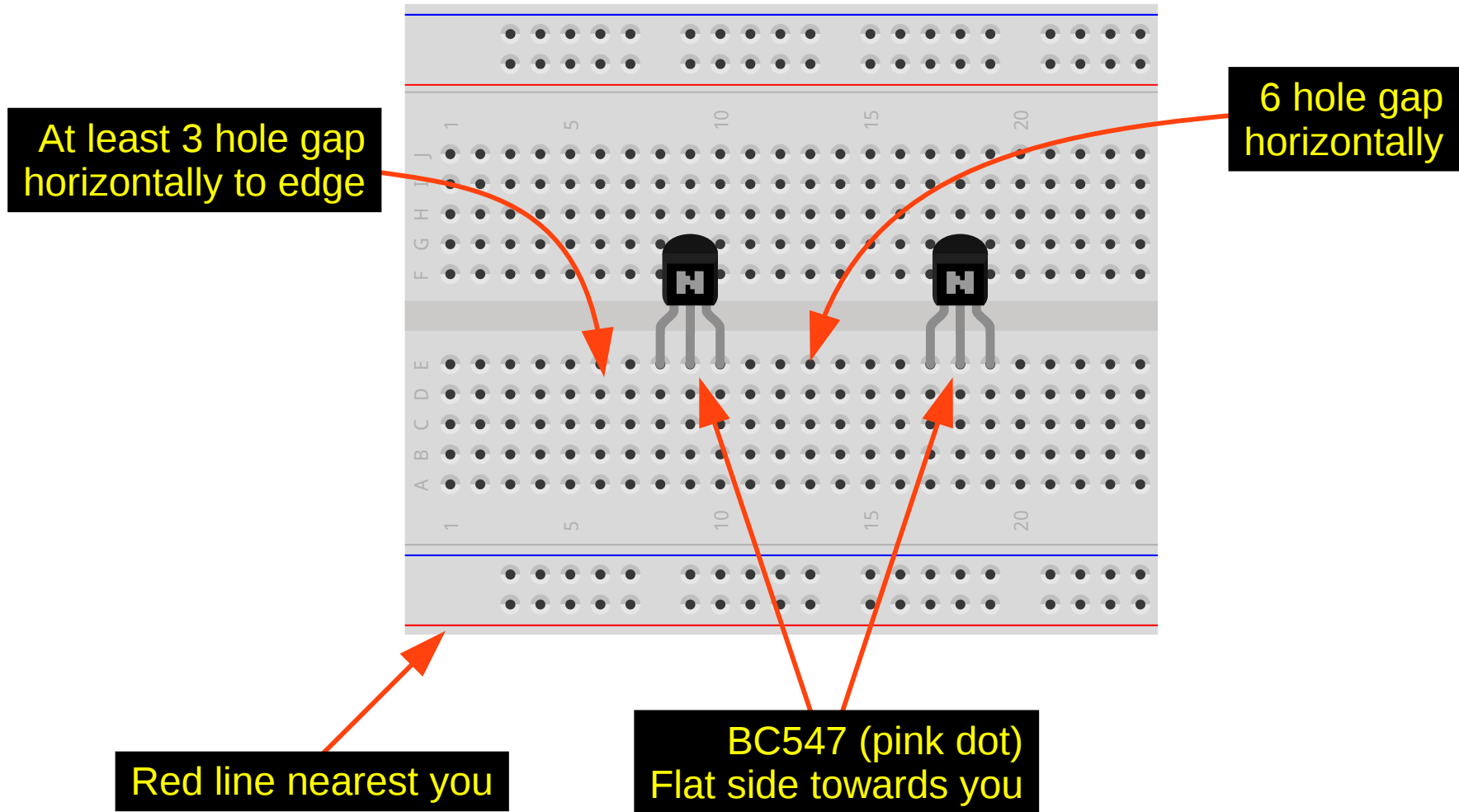


Bistable – Step 2

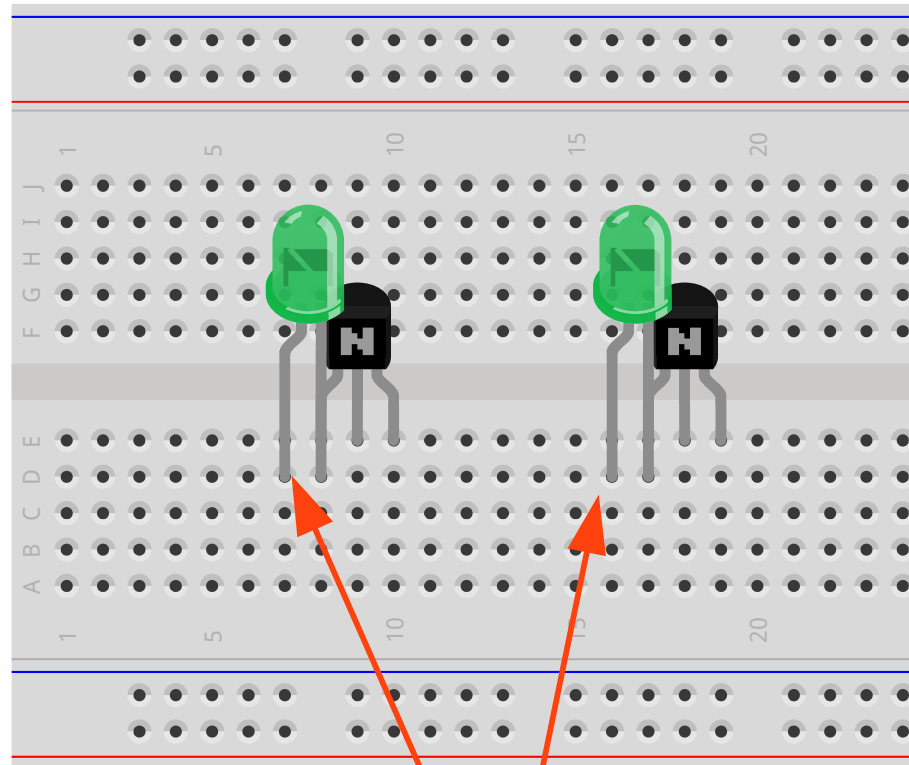

LED: cathode on right
(flat side, short leg)


Bistable – Step 3

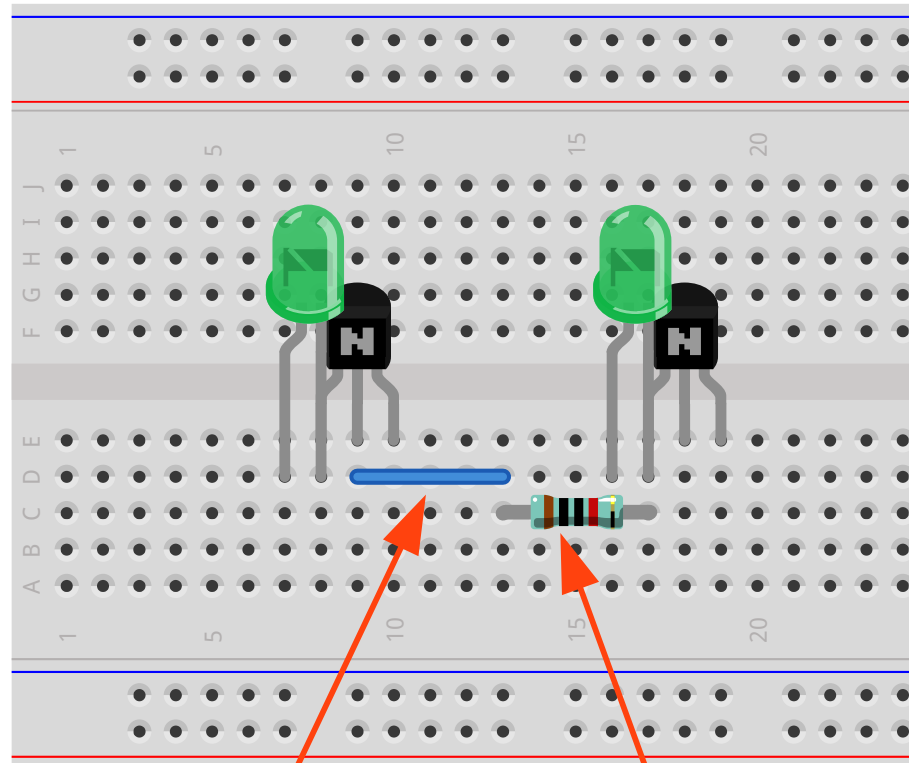

Wire

10kΩ resistor
Brown, black, black, red


Bistable – Step 4

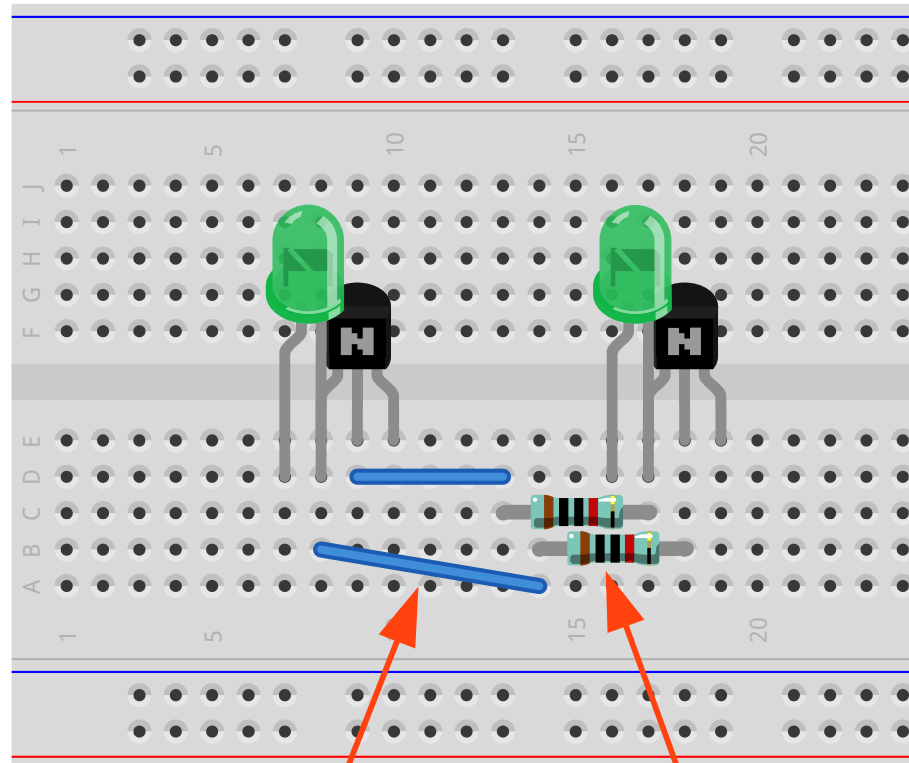


Wire

10kΩ resistor
Brown, black, black, red

Bistable – Final

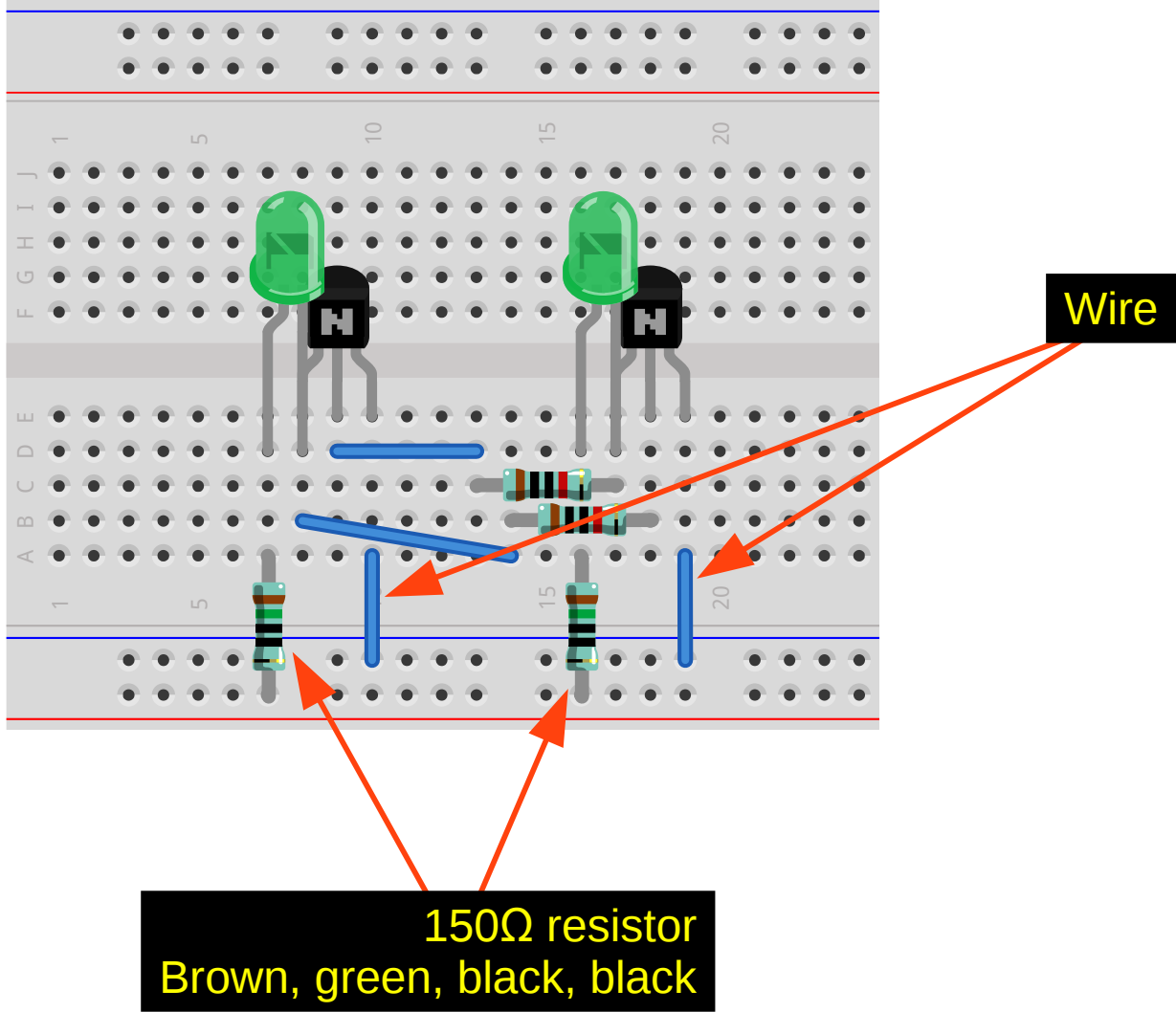


Bistable – Test

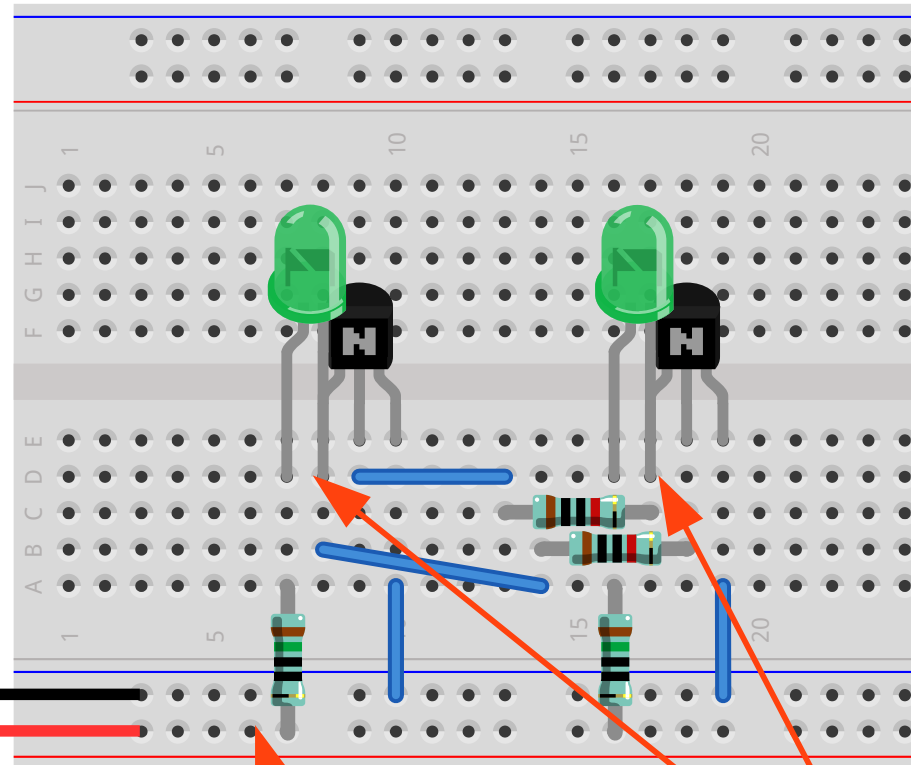


Apply power
Match heat-shrink colors

Touch wire from POWER ... to either LED's right pin
One pin at a time


Monostable Circuit

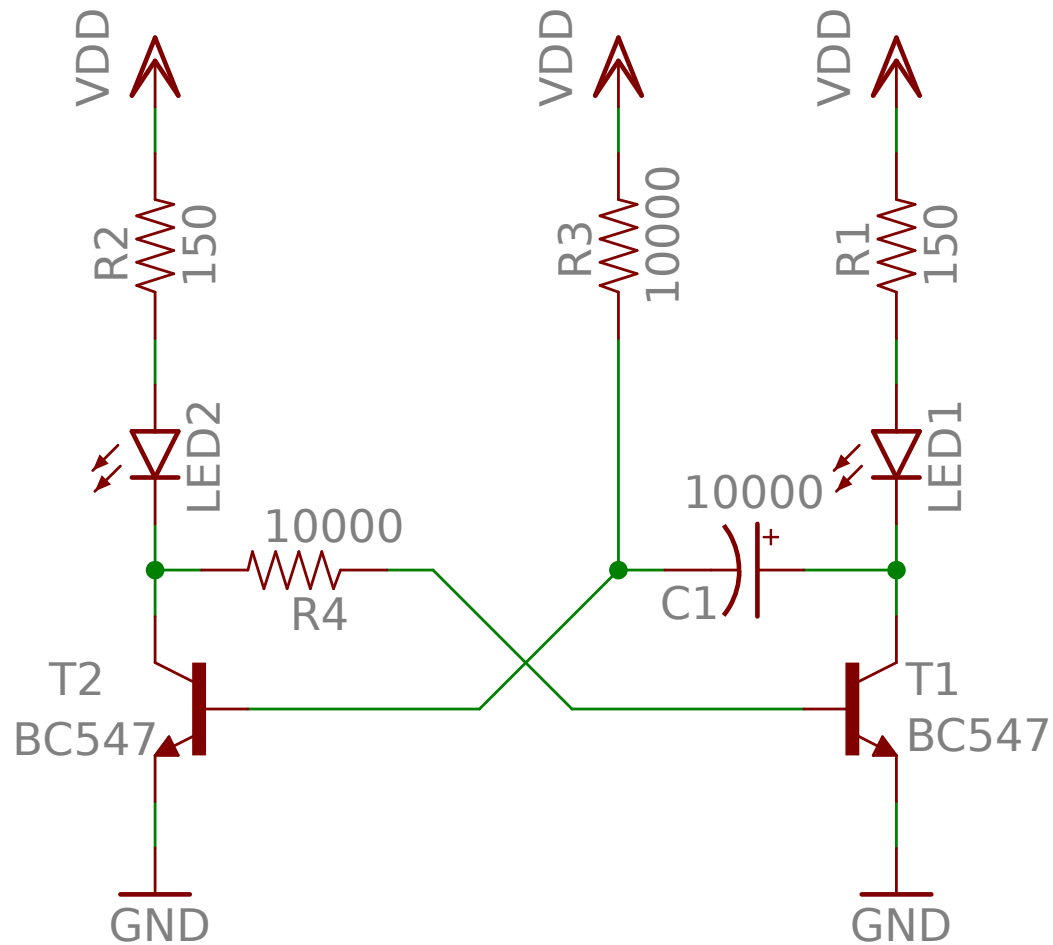


Monostable Circuit

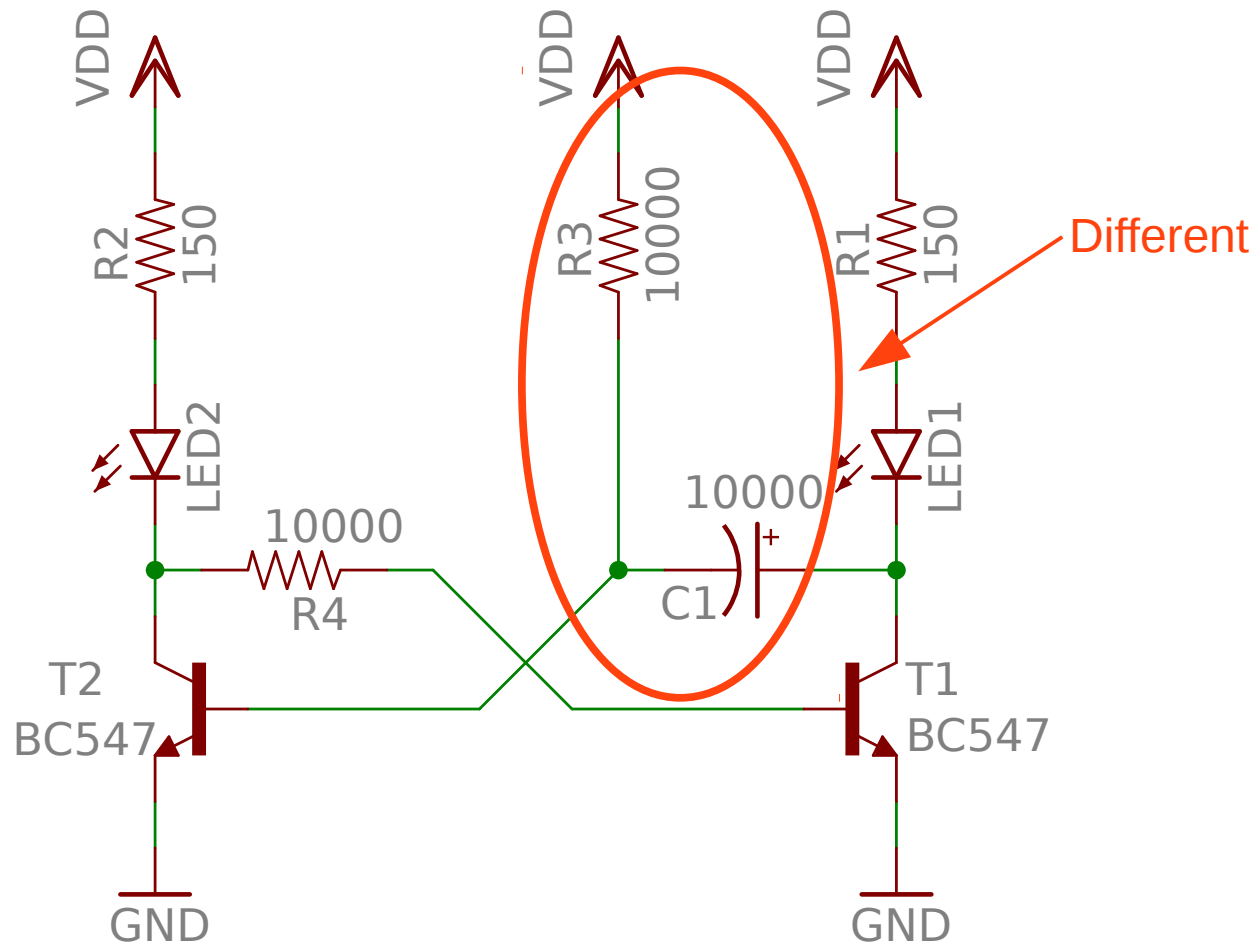


Monostable Circuit – Stable State

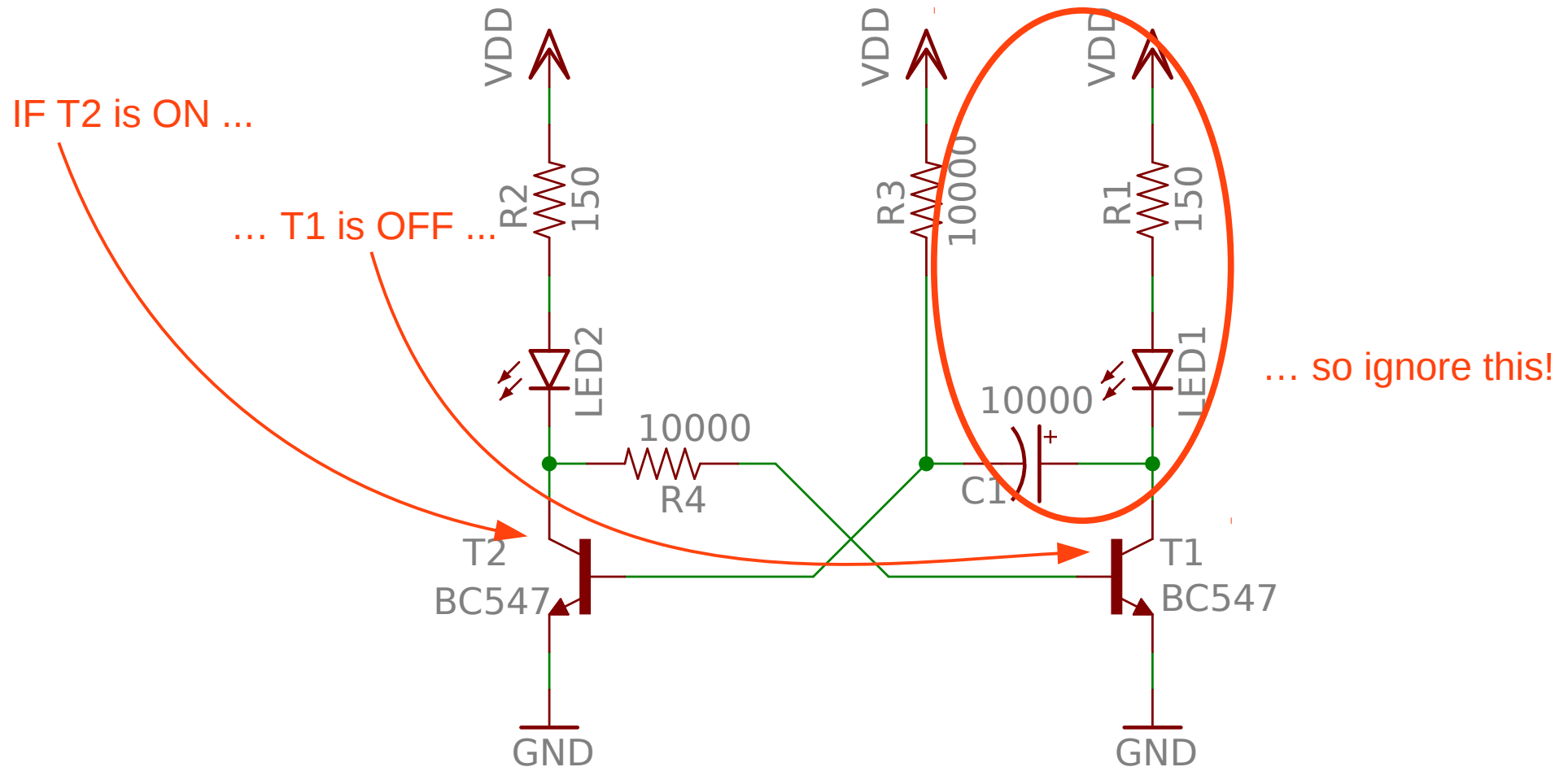


Monostable Circuit – Unstable State

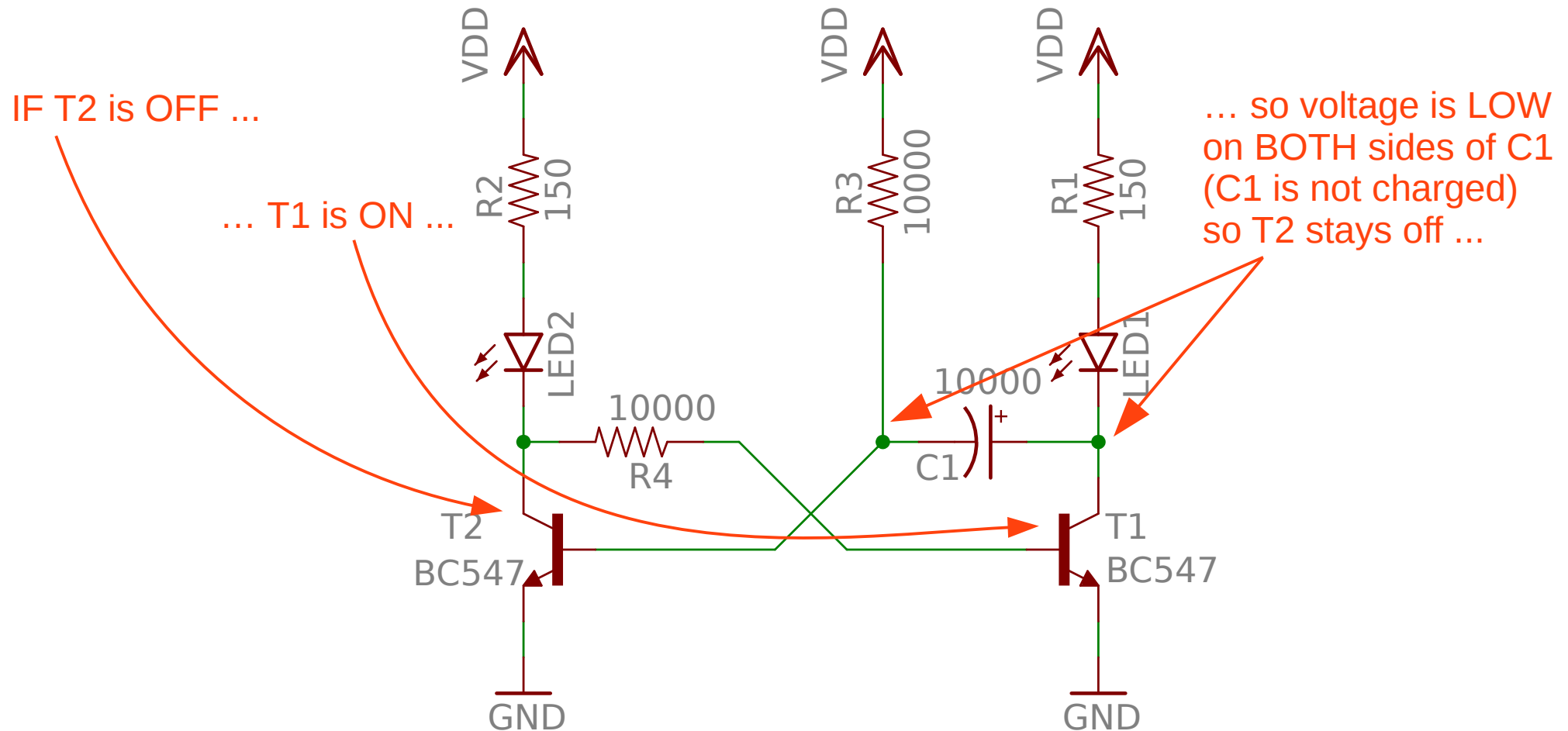

Monostable Circuit – Unstable State

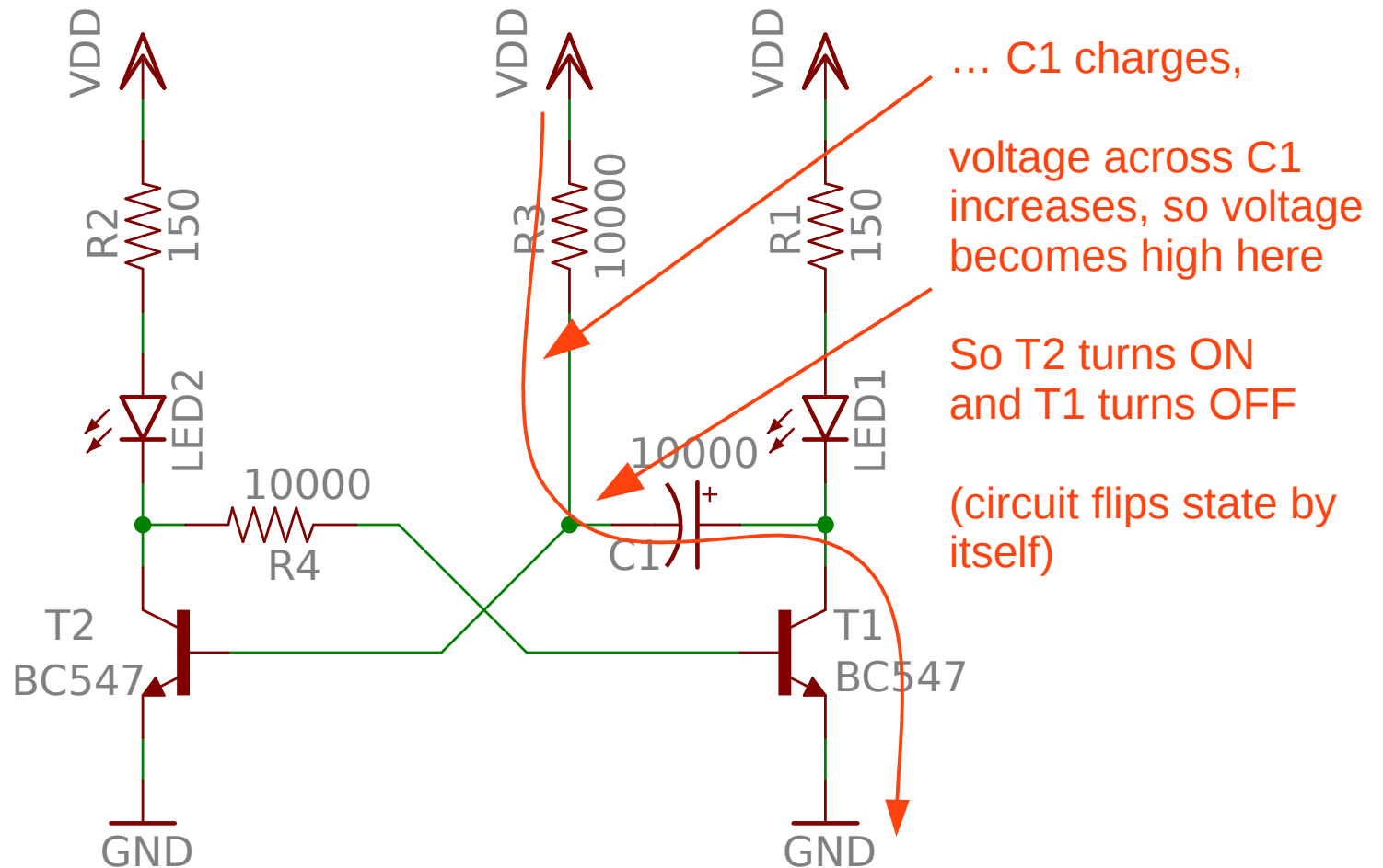


Monostable Circuit – Unstable State

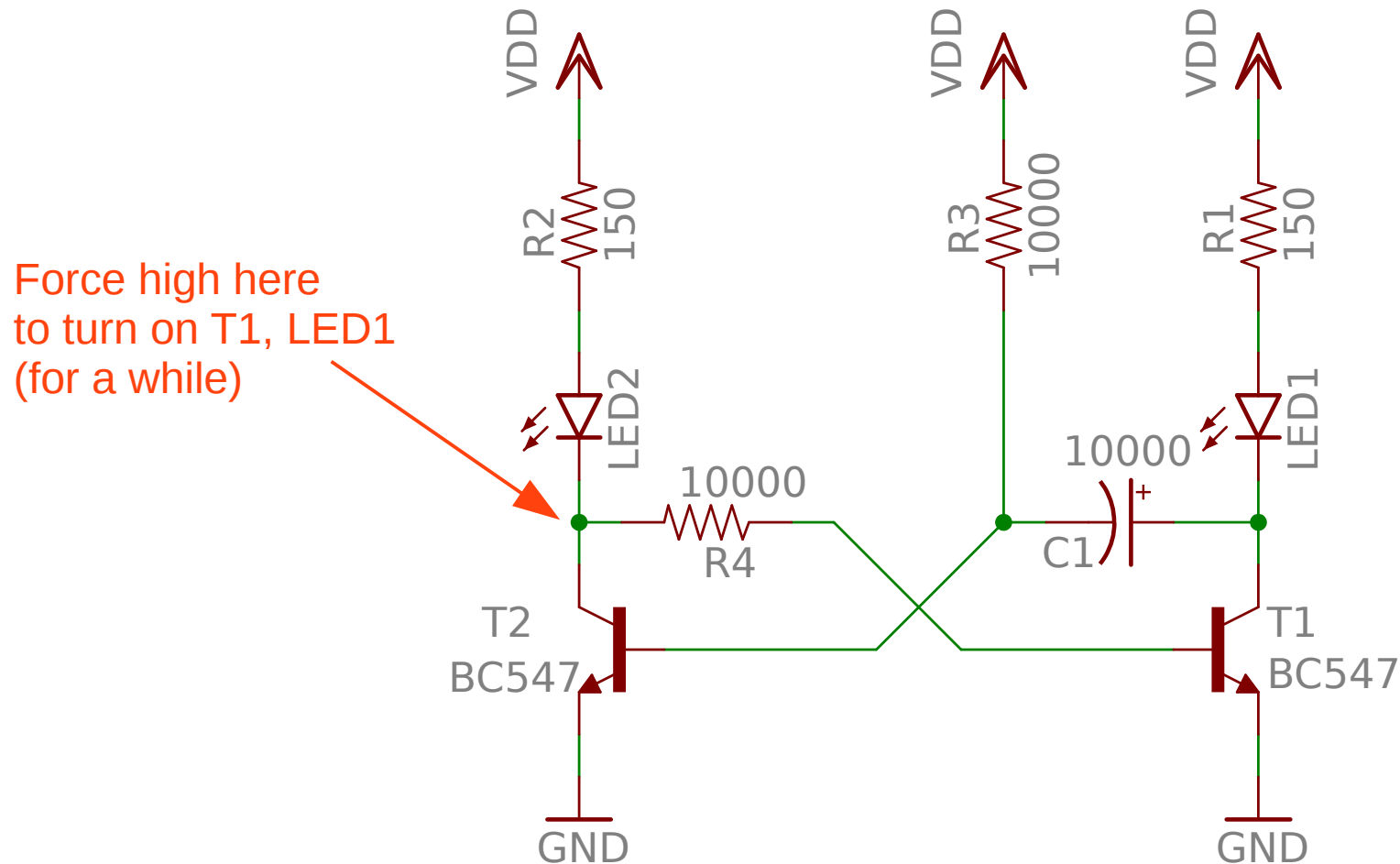


Monostable Animation

<http://www.falstad.com/circuit/e-multivib-mono.html>

Monostable – Step 1

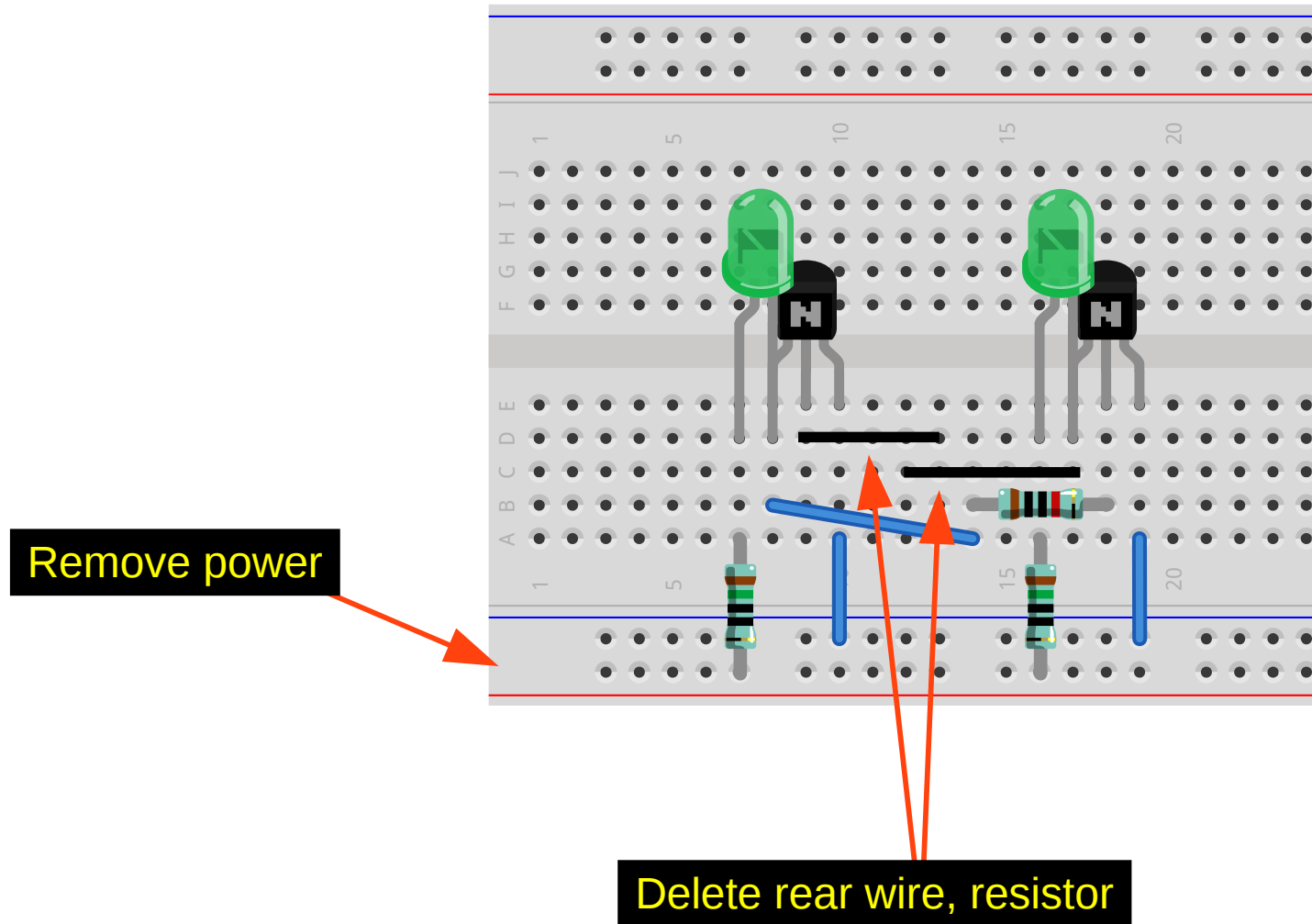


Monostable – Step 2

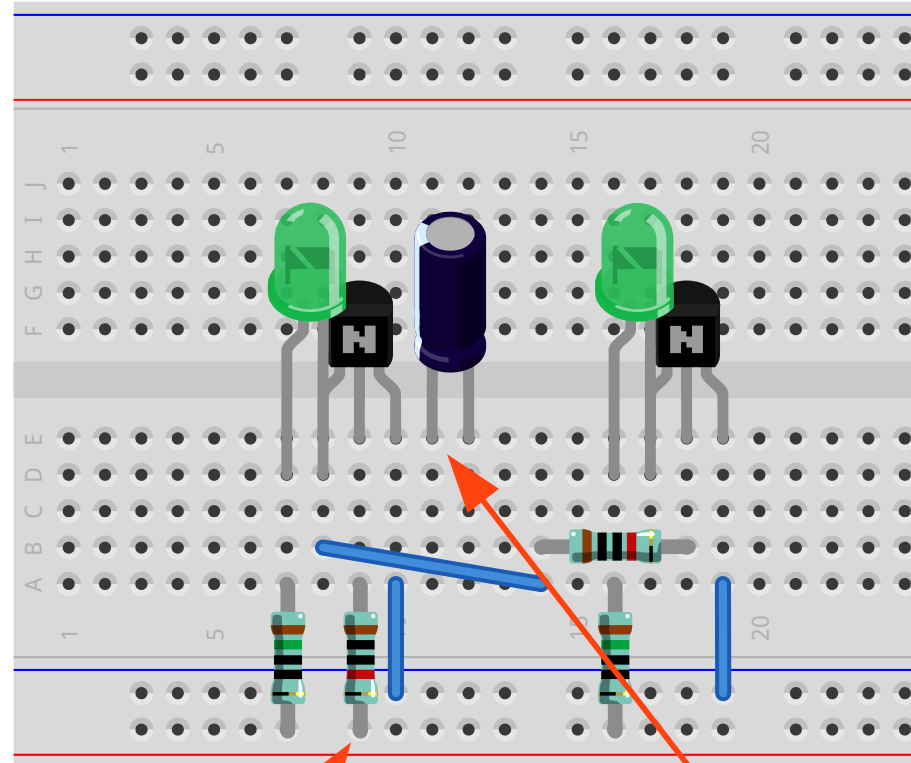


10kΩ resistor
Brown, black, black, red

10μF capacitor
Negative pin (stripe) on left

Monostable – Final

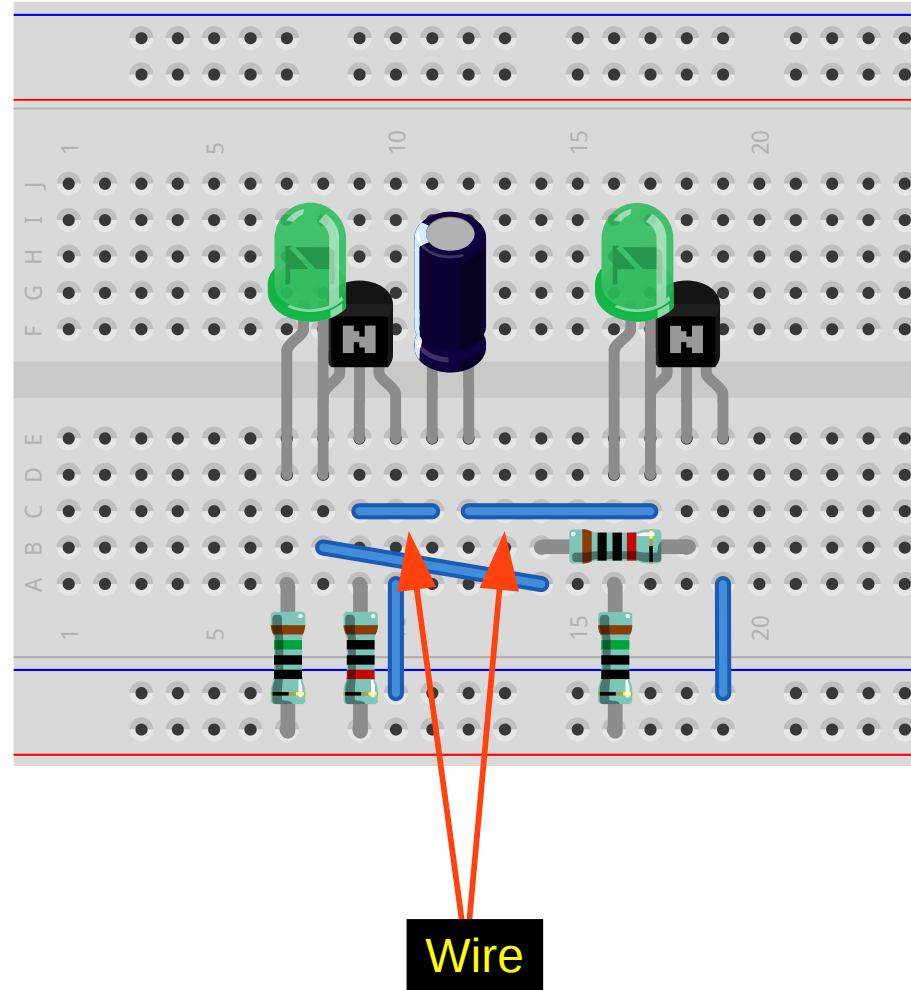


Monostable – Test

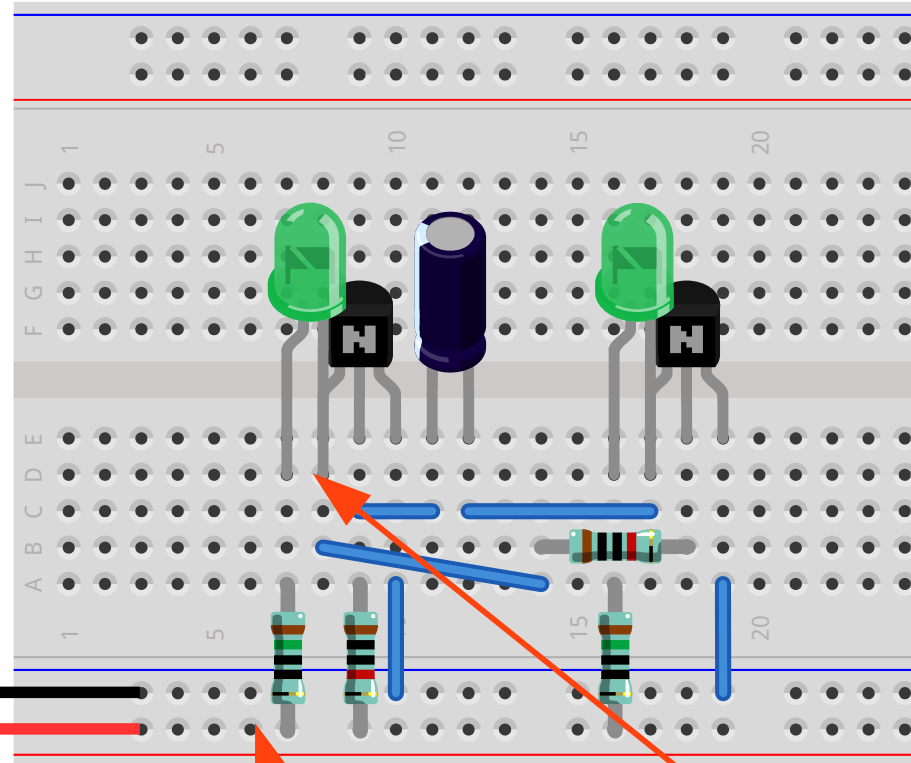


Apply power
Match heat-shrink colors

Touch wire from POWER ... to left LED's right pin
Wait for LEDs to change automatically


Astable Circuit

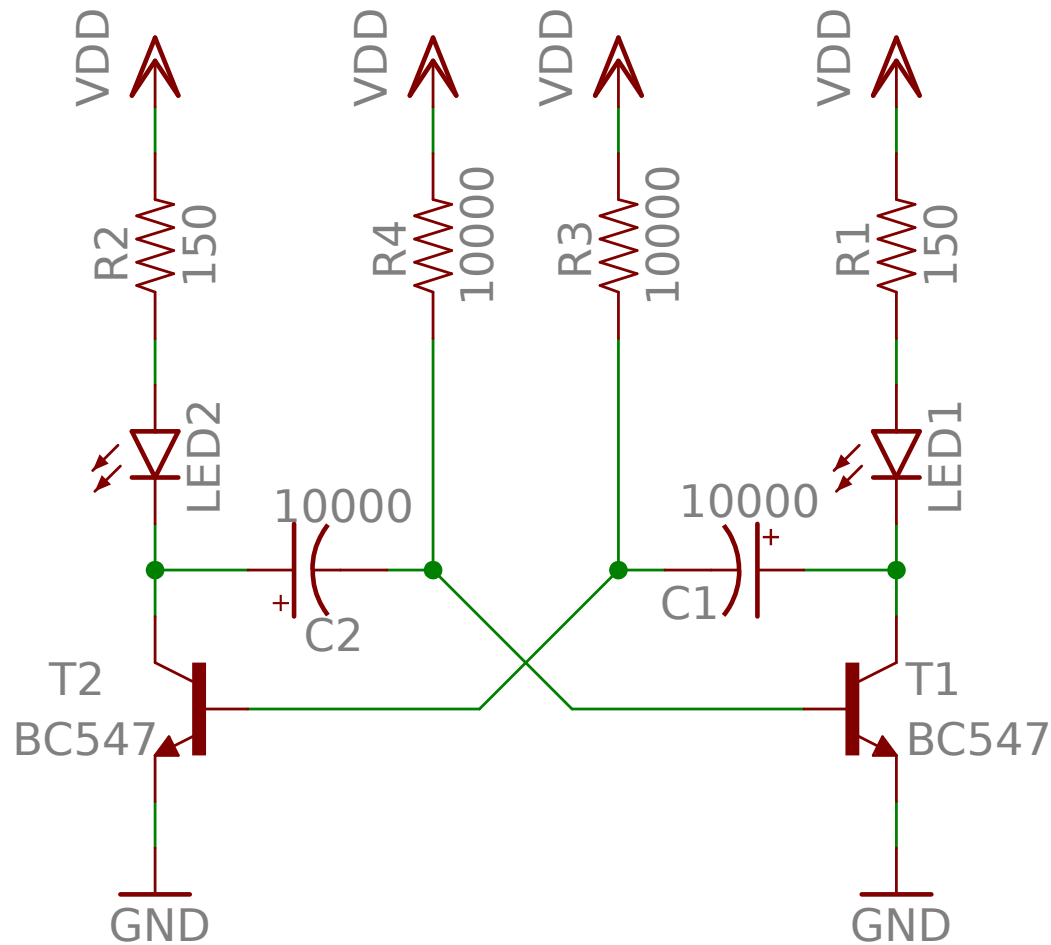


Astable Circuit

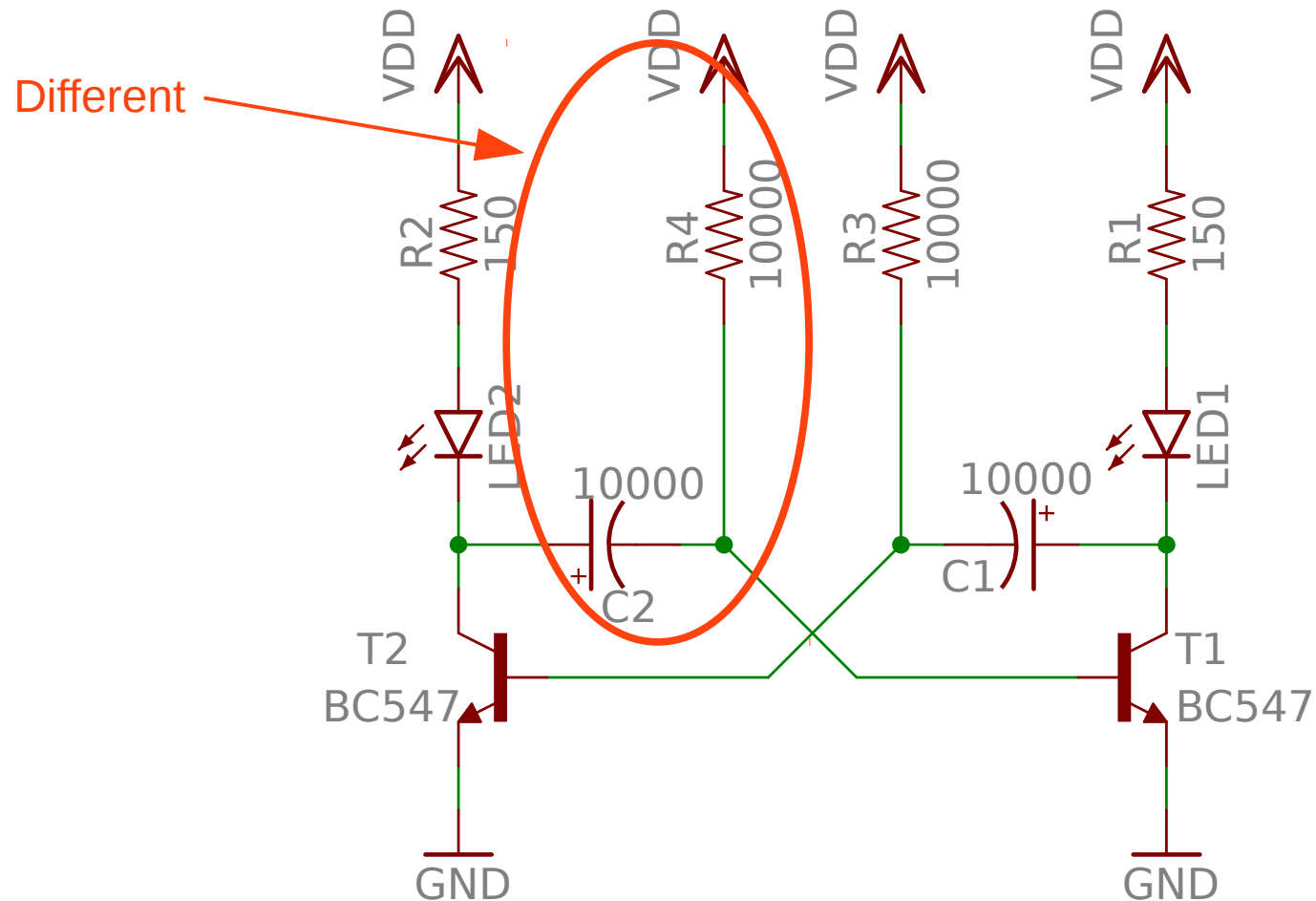

Astable Circuit – Unstable state 1

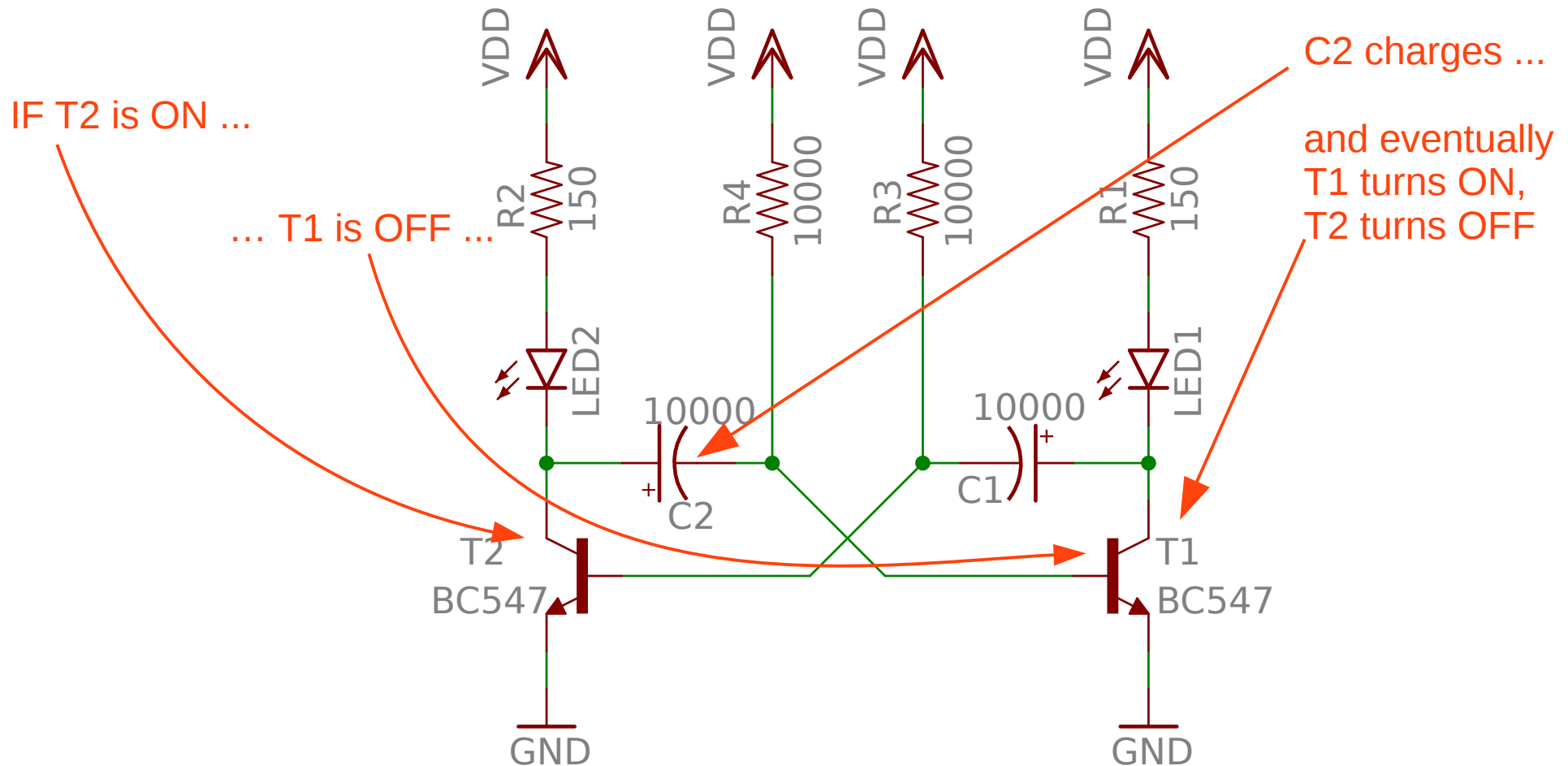

Astable Circuit – Unstable state 2

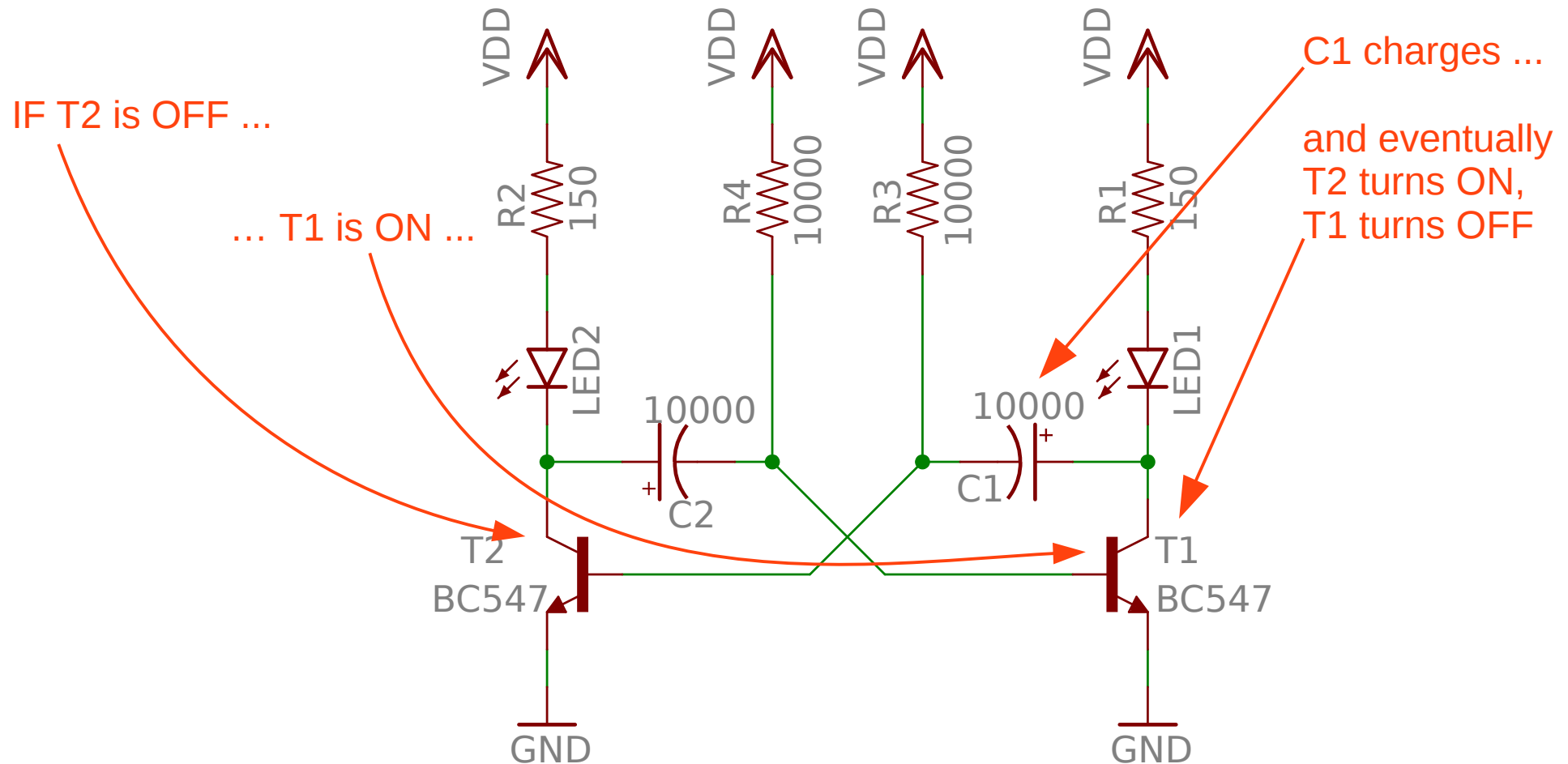


Astable Animation

<http://www.falstad.com/circuit/e-multivib-a.html>


Astable – Step 1

Remove power

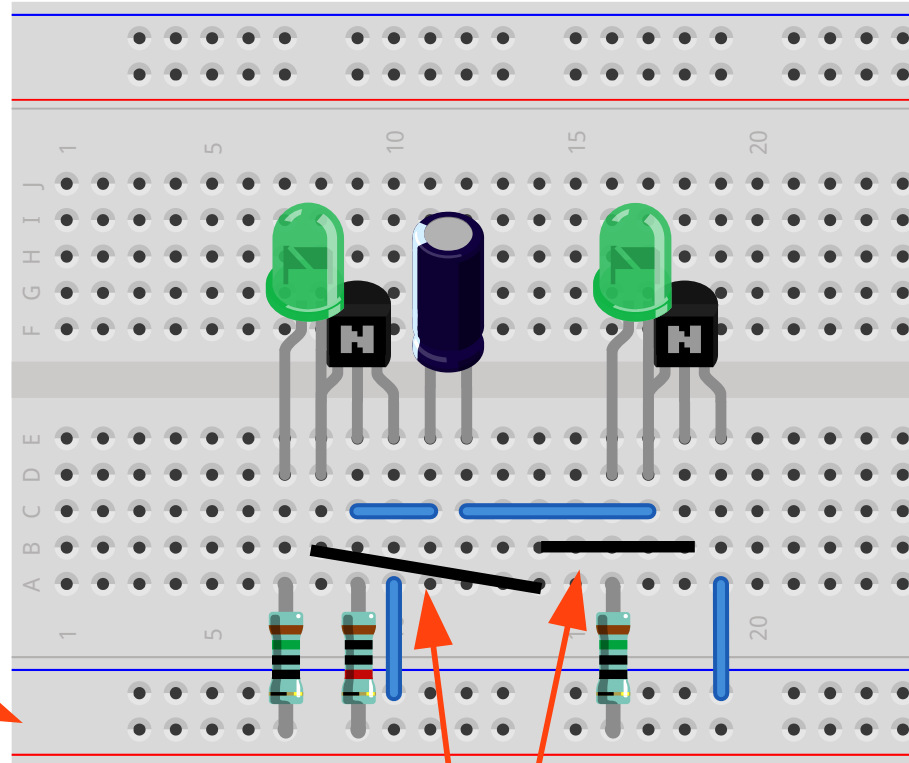

Delete front wire, resistor


Astable – Step 2

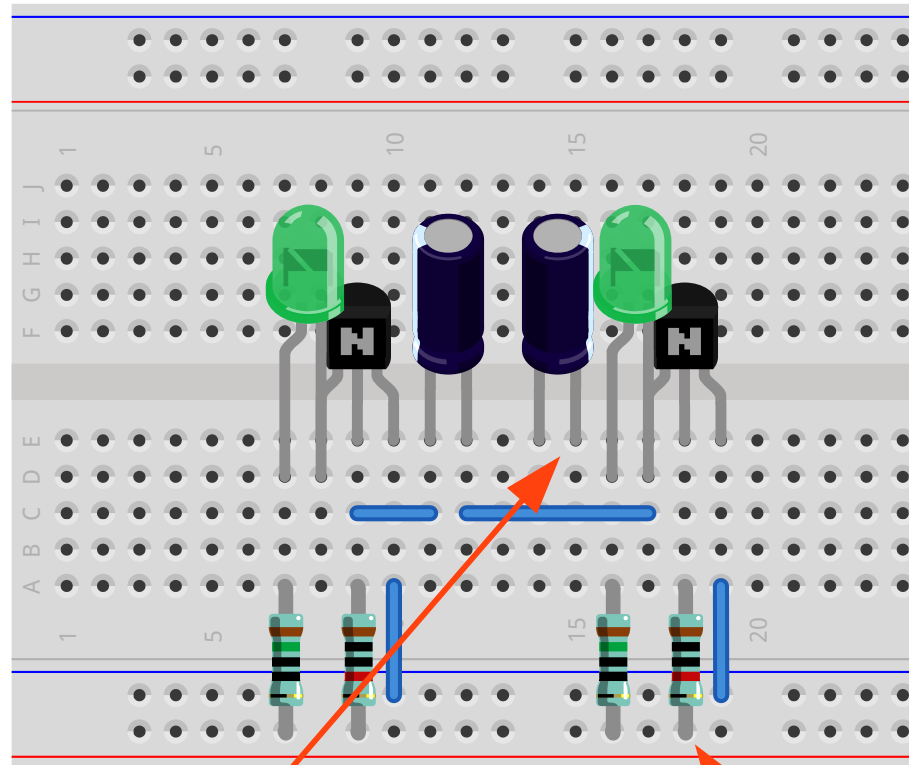

10μF capacitor
Negative pin (stripe) on right


10kΩ resistor
Brown, black, black, red

Astable – Final

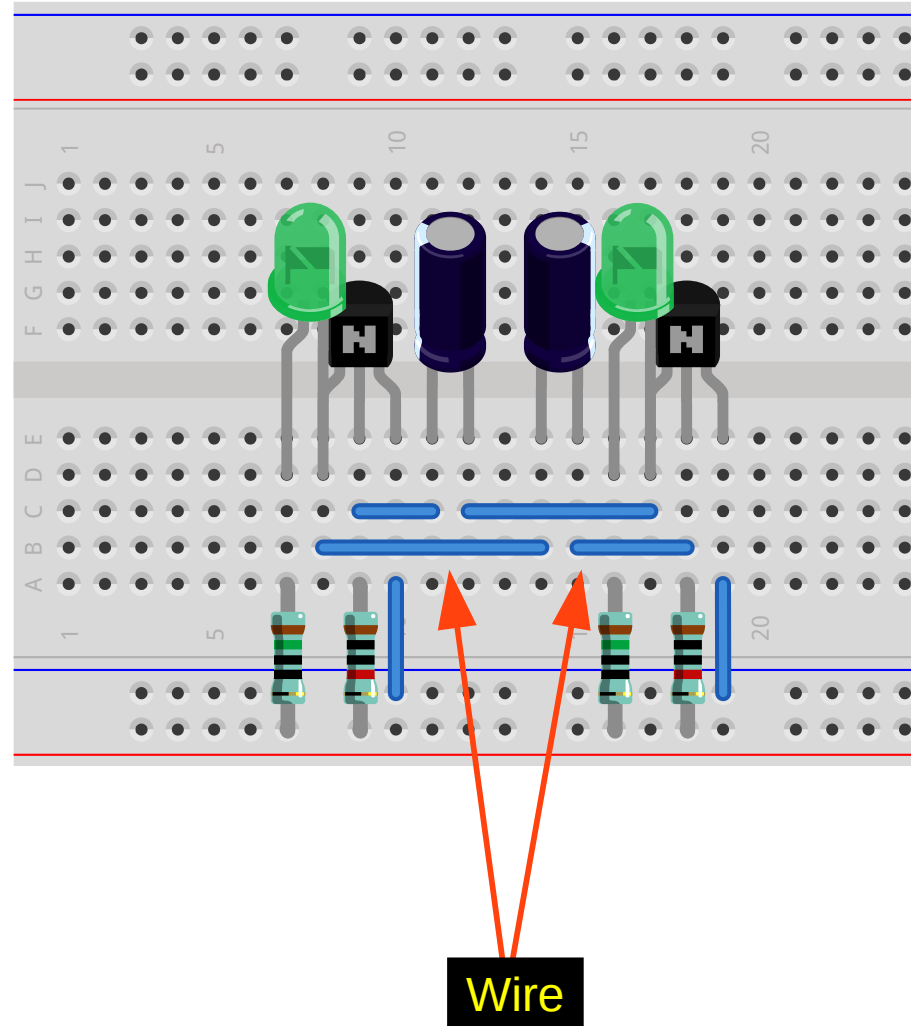

Astable – Test

Apply power
Match heat-shrink colors

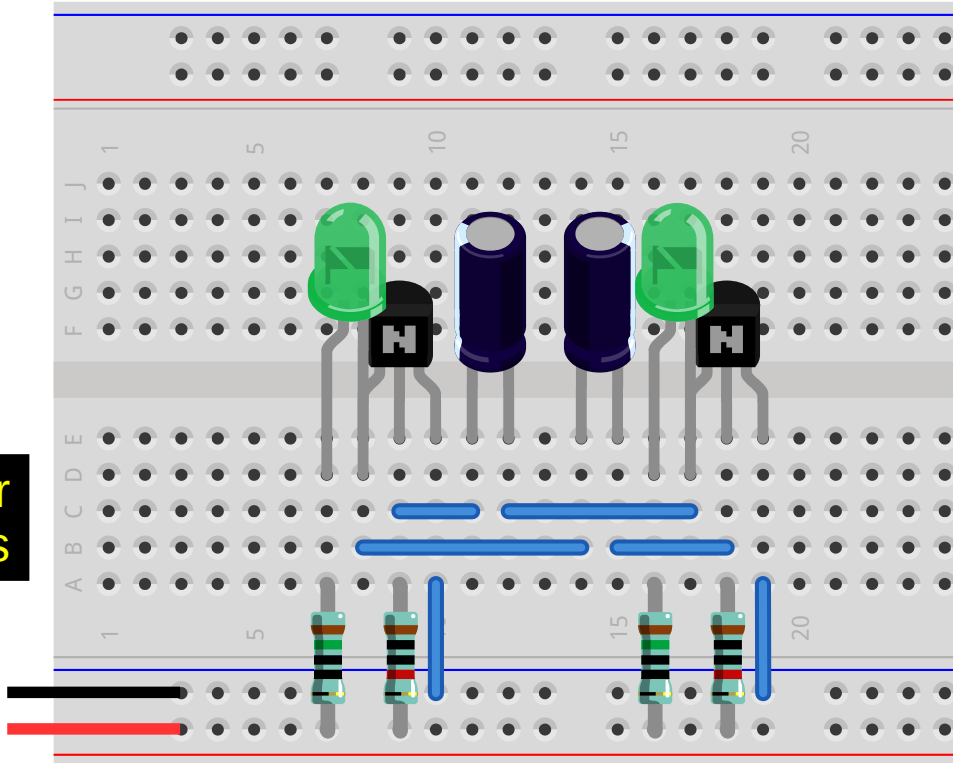

Observe circuit switching back and forth
between two states automatically

Questions

(and congratulations for
getting through nearly 50 slides!)