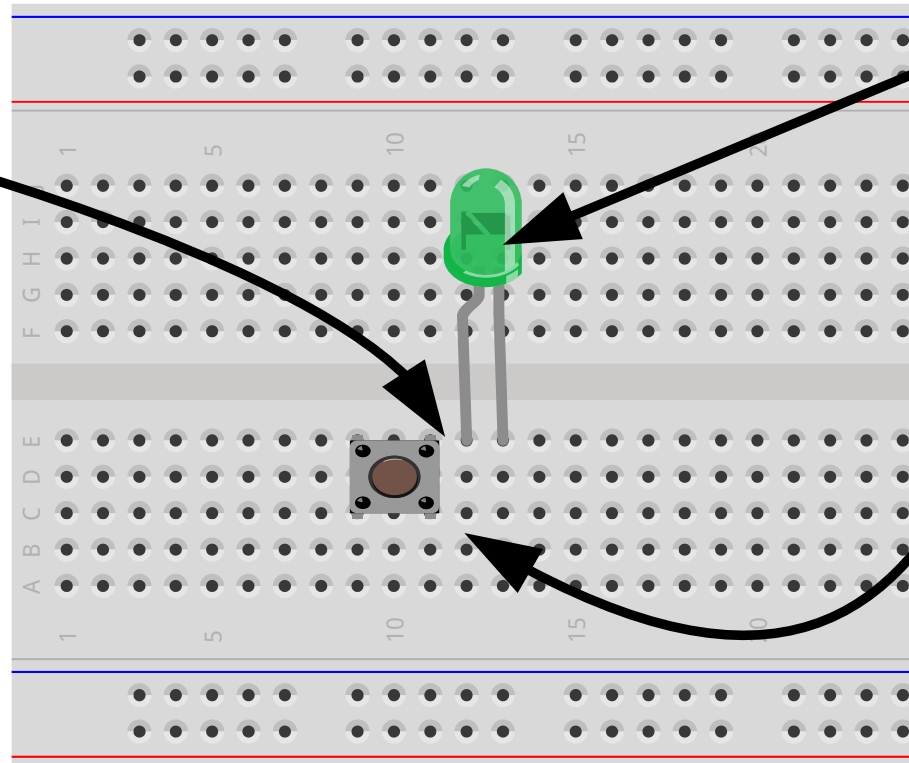


NOT gate – Step 1

Both components far back against gutter

Components are adjacent, not sharing columns




LED:

Flat side, short lead on right


Switch:

Wires stick out of top and bottom of switch, not left and right

NOT gate – Step 2

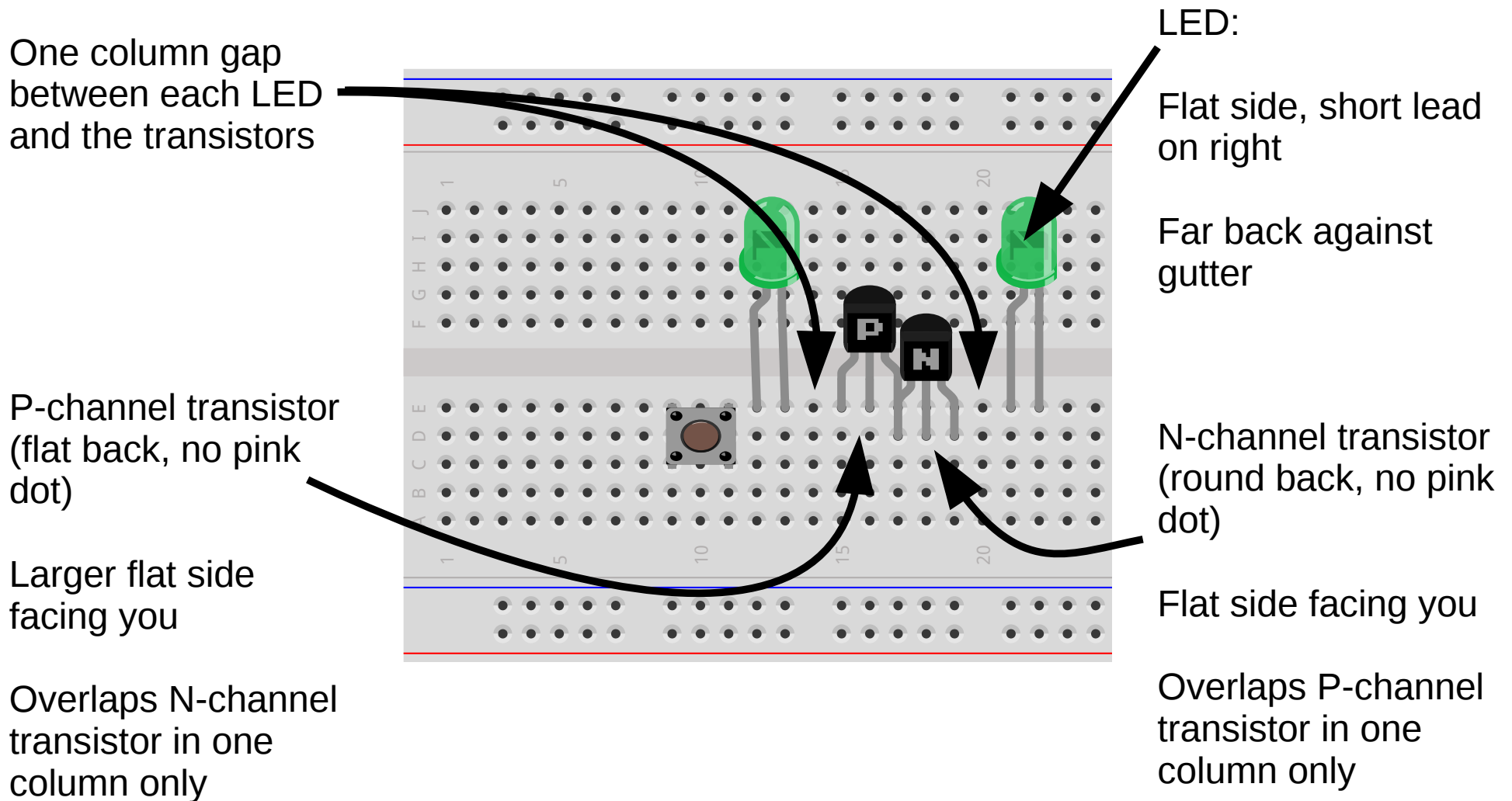


NOT gate – Step 3

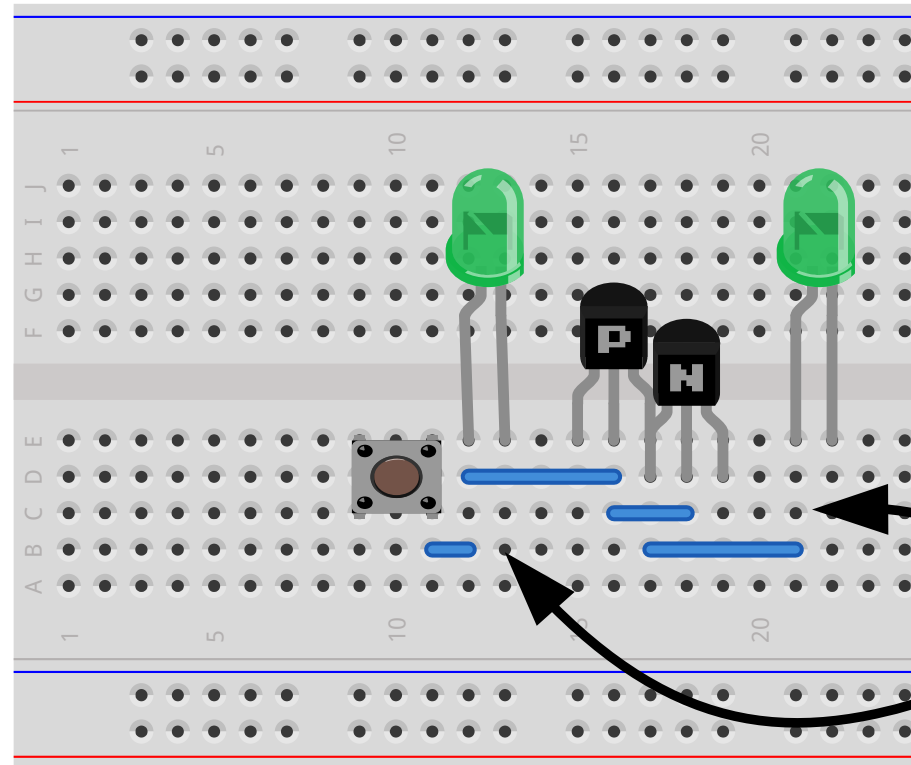

Add four Wires

Pay careful attention
to exactly match the
picture

NOT gate – Step 4

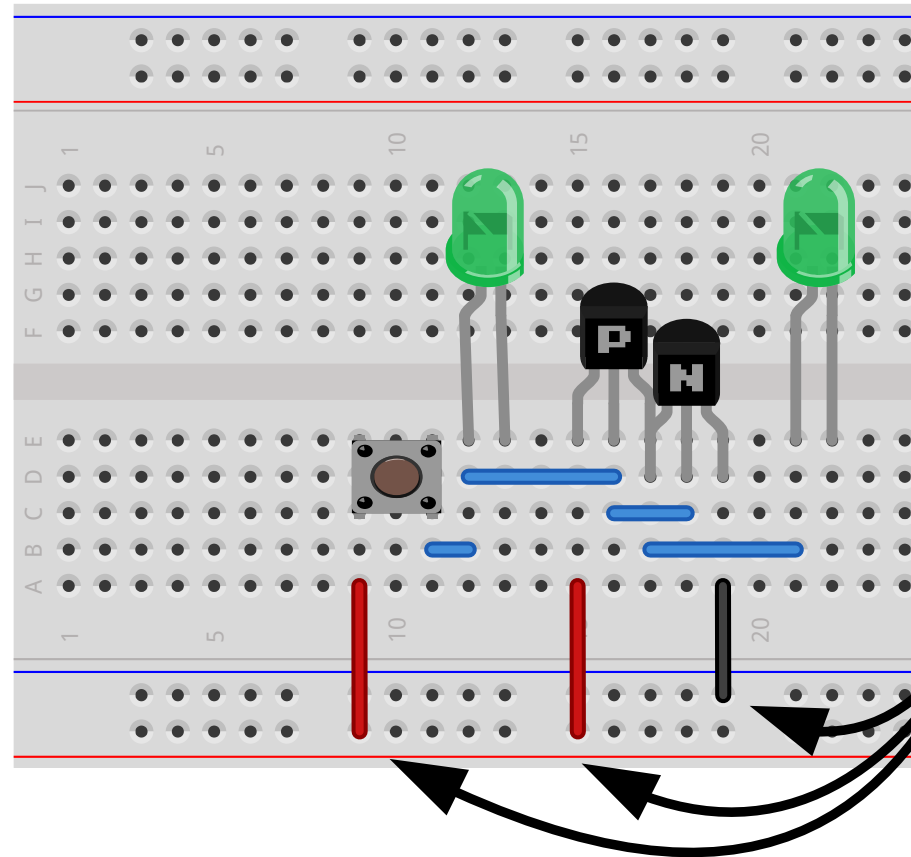

Add three Wires


Pay careful attention
to exactly match the
picture

NOT gate – Step 5

Resistor 10K Ω :

Brown black black
red

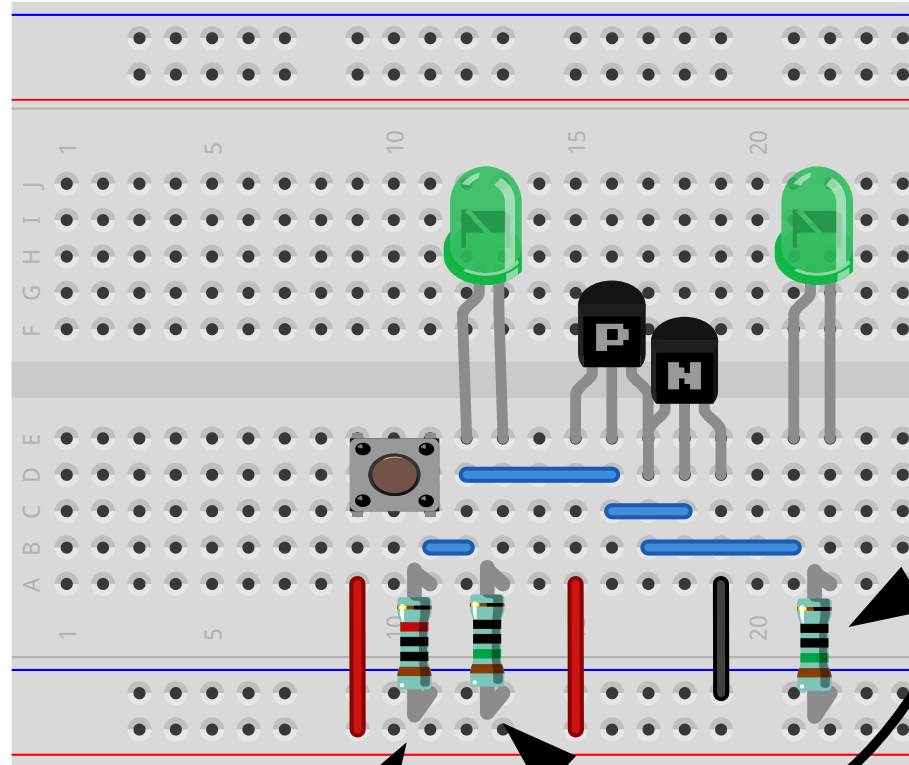In the same column
as the switch's right
wires



Resistor 150 Ω :

Brown green
black black


In the same column
as each LED's right
wire

NOT gate – Step 6

Plug in power once circuit is complete

Pay attention to the colors of the two wires

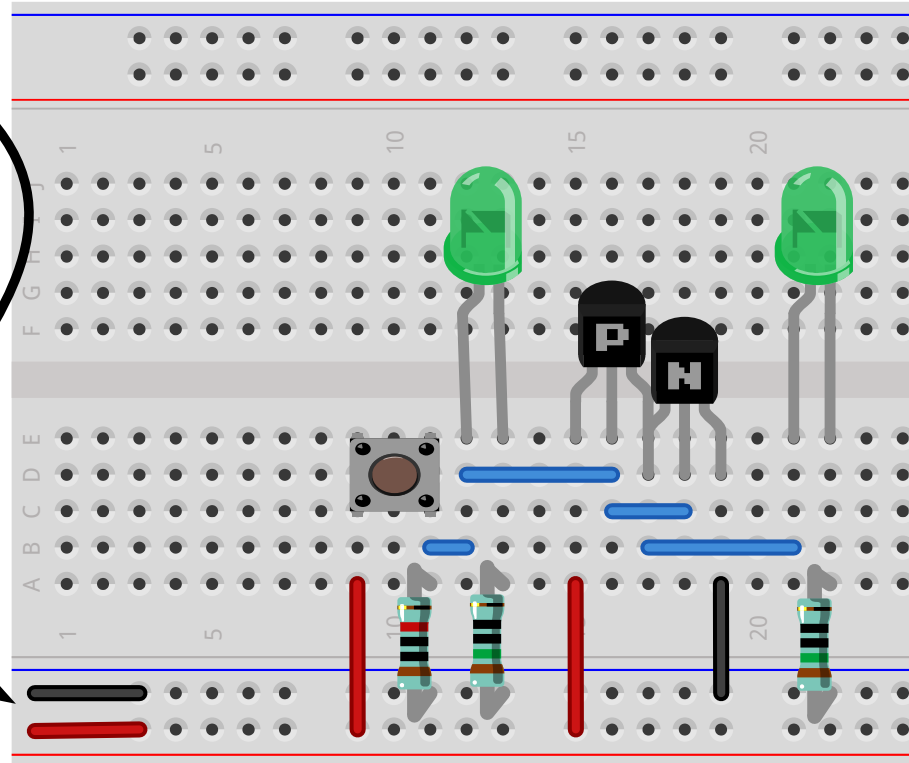Observe the two LEDs' behavior when the switch is pressed and released



NOT gate – Analysis

- The left LED is the circuit's input
- The right LED is the circuit's output
- When the switch is not pressed, what state are the input and output? (Each is “on” or “off”)
- When the switch is pressed, what state are the input and output now?
- How does the output relate to the input? (unrelated, always on, always off, same, or opposite)