
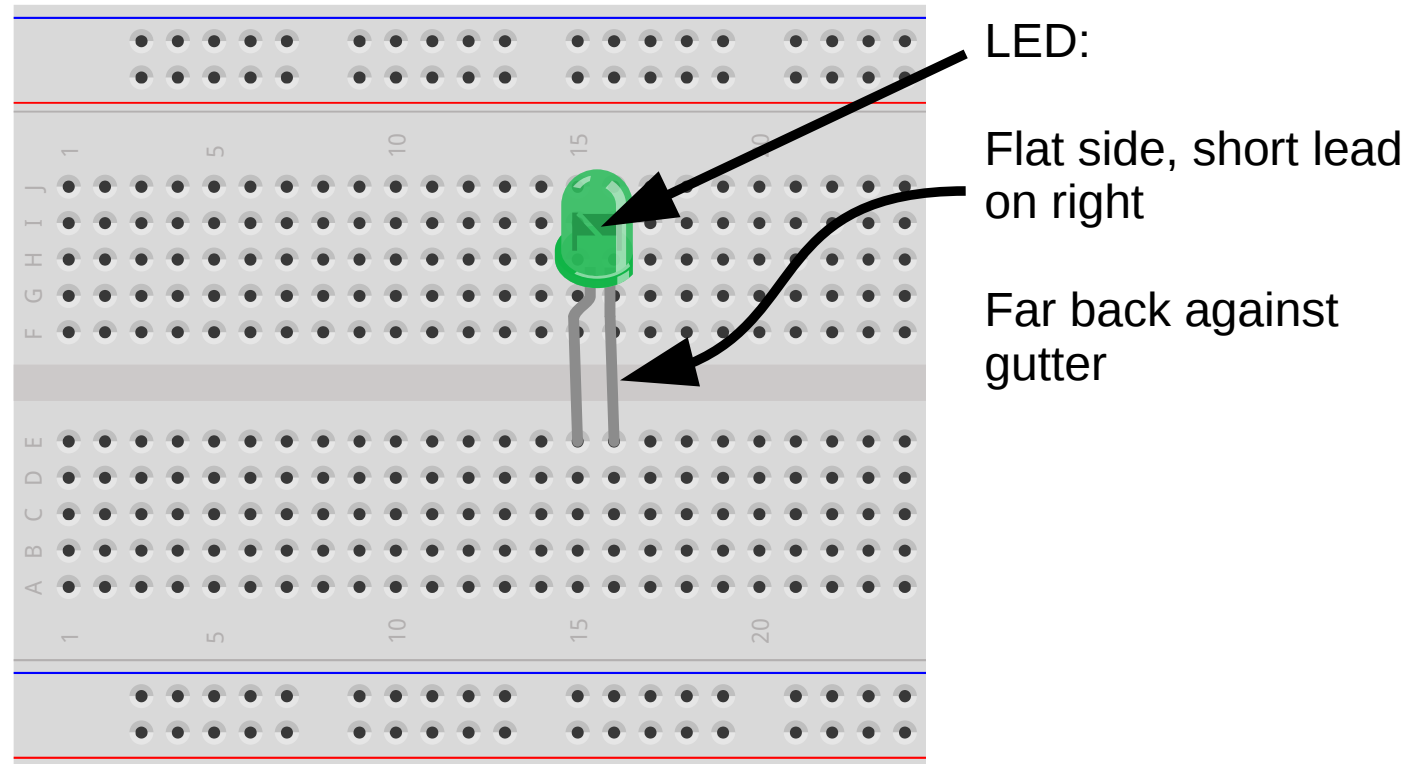



# LED and Switch – Step 1

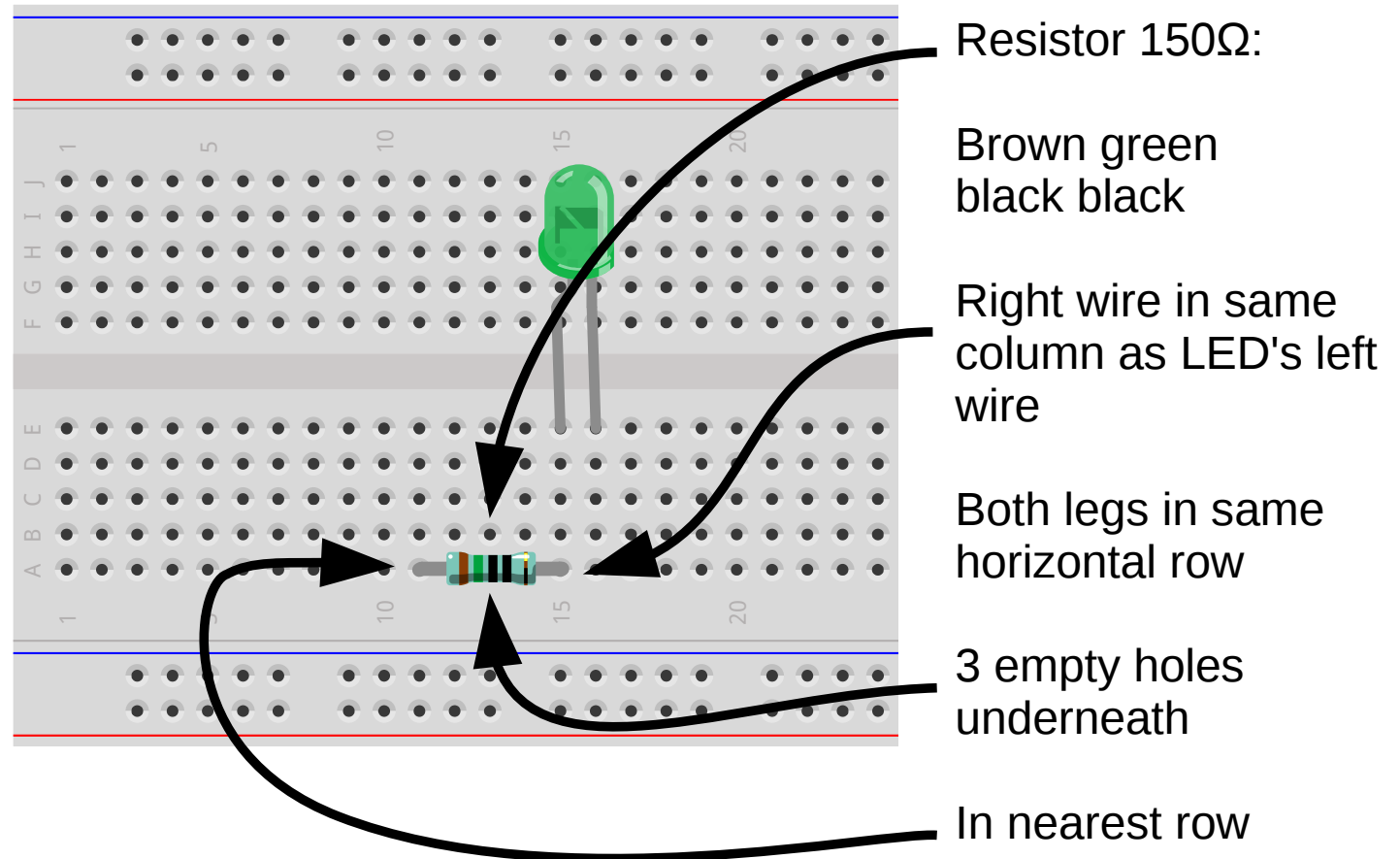

# LED and Switch – Step 2



# LED and Switch – Step 3

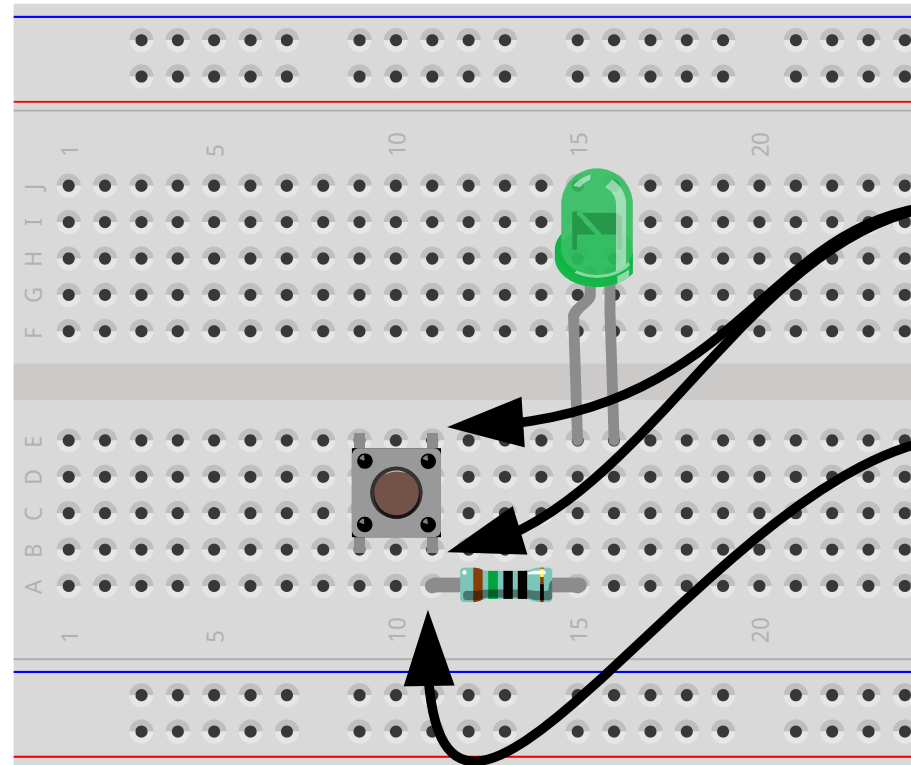


Push switch:

Wires stick out of top and bottom of switch, not left and right

Right wires in same column as resistor's left wire

# LED and Switch – Step 4

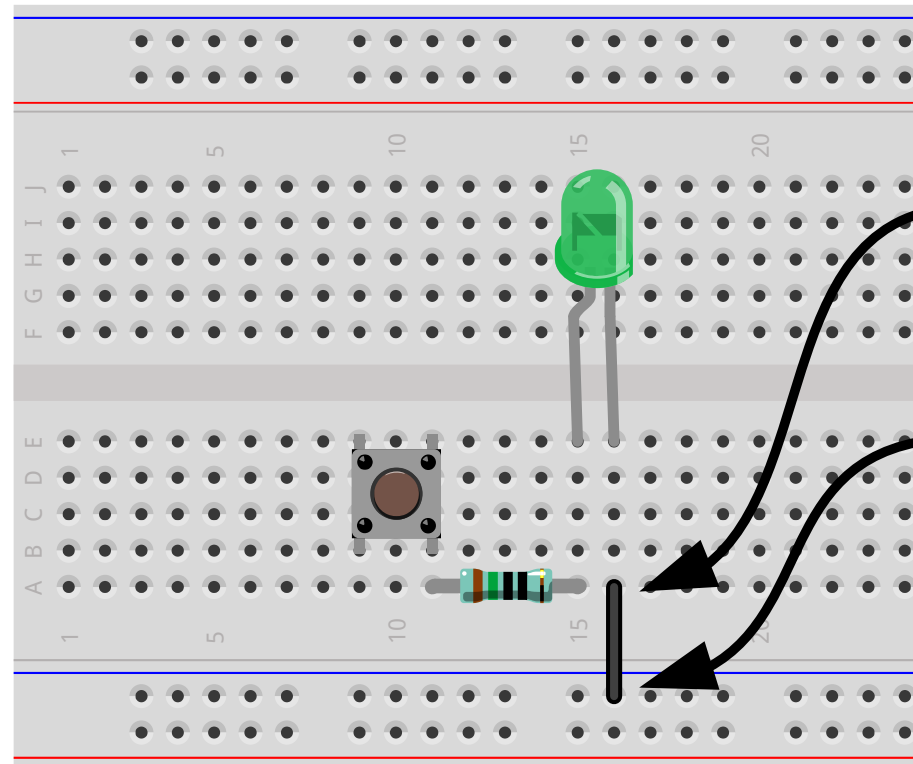


Wire:

Top end aligns vertically with LED's right wire

Bottom end in the power rail that's farther away from you

# LED and Switch – Step 5

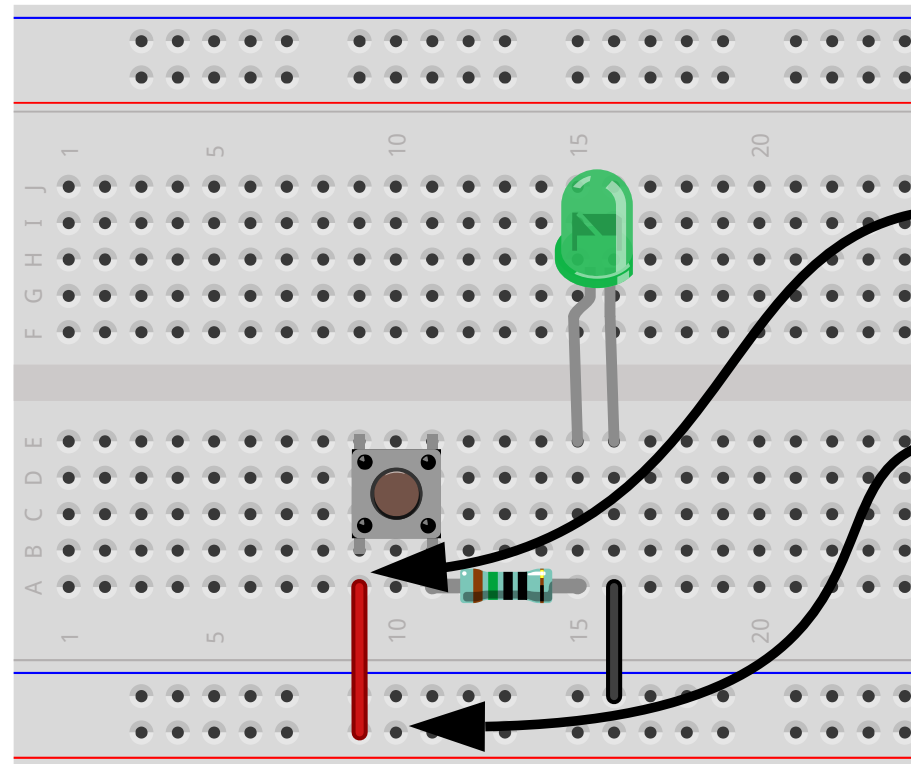

Wire:

Top end aligns vertically with push switch's left wire

Bottom end in the power rail that's nearer to you

# LED and Switch – Step 6

Plug in power once circuit is complete

Pay attention to the colors of the two wires

Observe the LED light up when the push switch is pressed

