
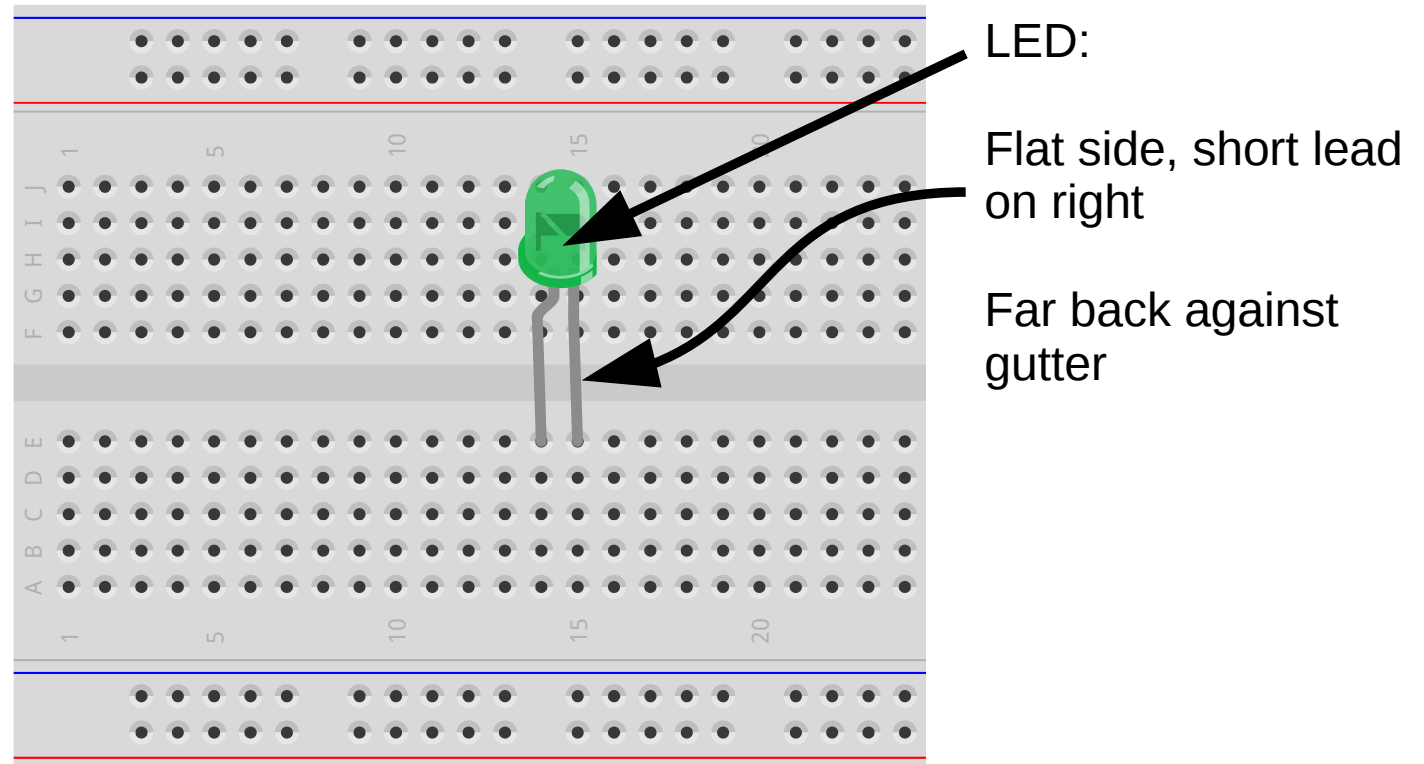



Light an LED – Step 1

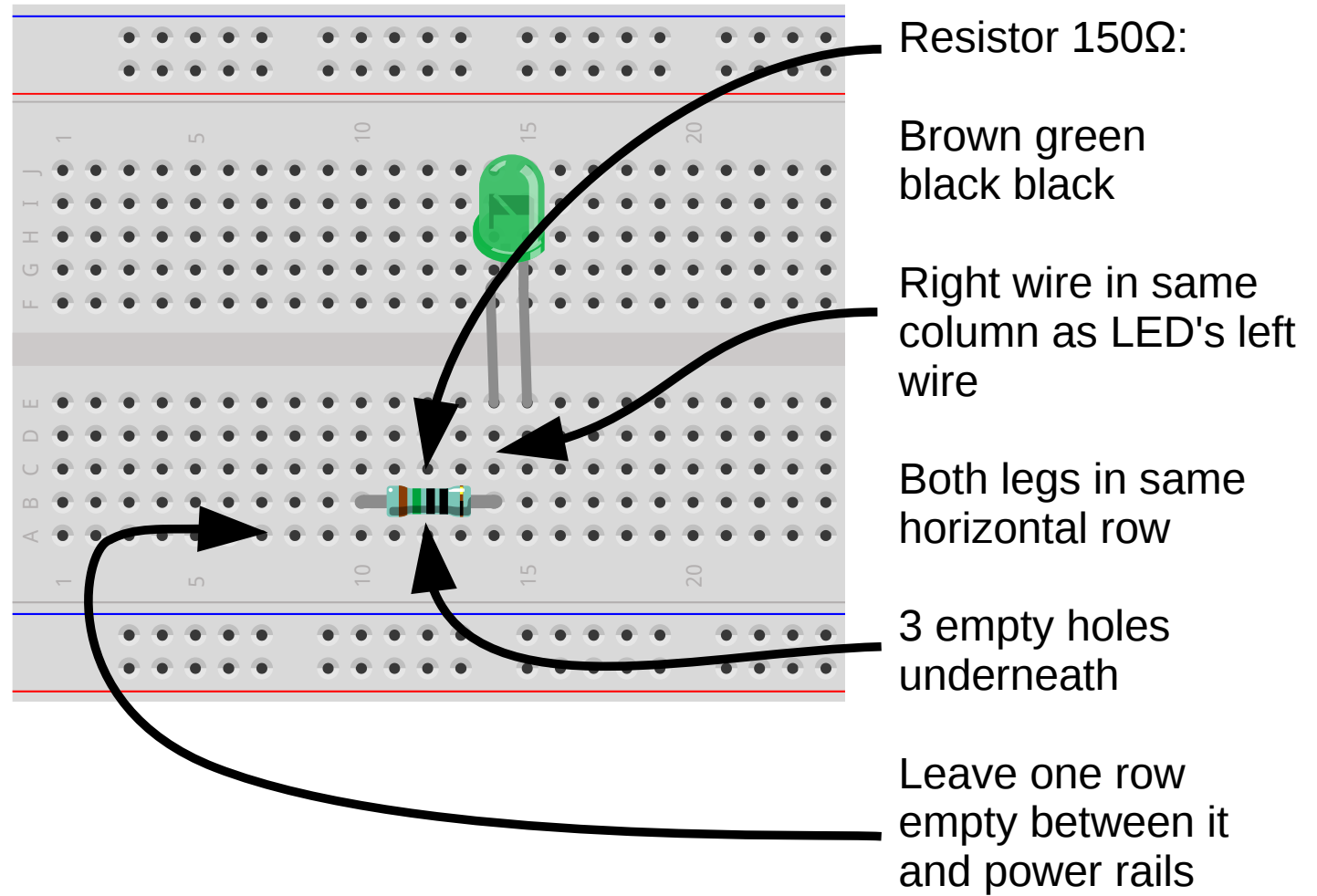

Light an LED – Step 2



Light an LED – Step 3

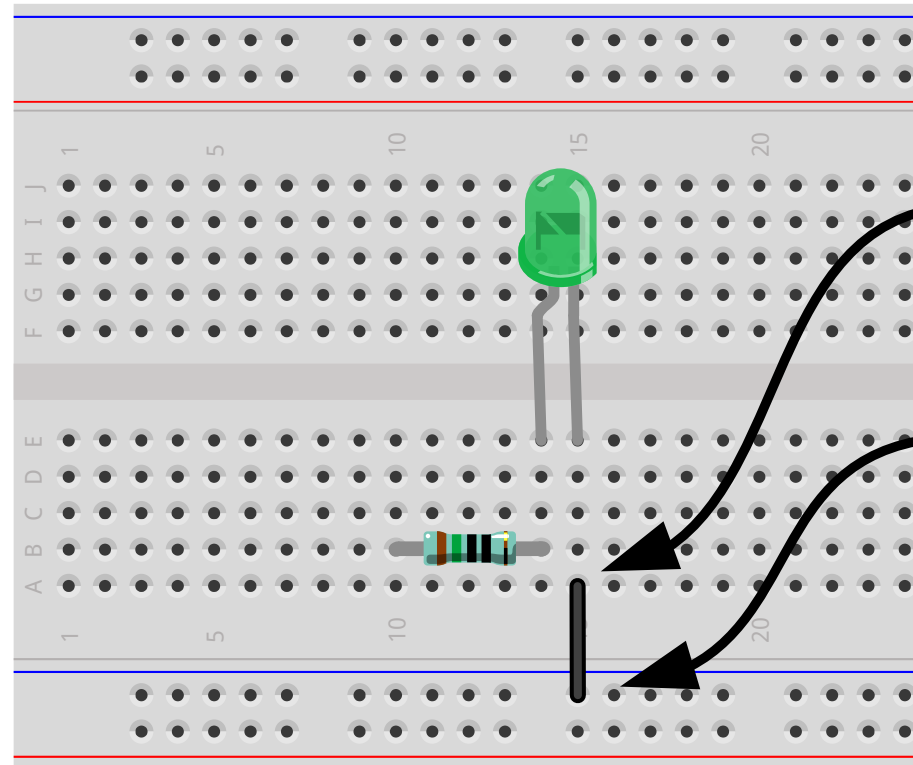

Wire:

Top end aligns vertically with LED's right wire


Bottom end in the power rail that's farther away from you

Light an LED – Step 4

Plug in power once circuit is complete

Pay attention to the colors of the two wires

Observe the LED light up

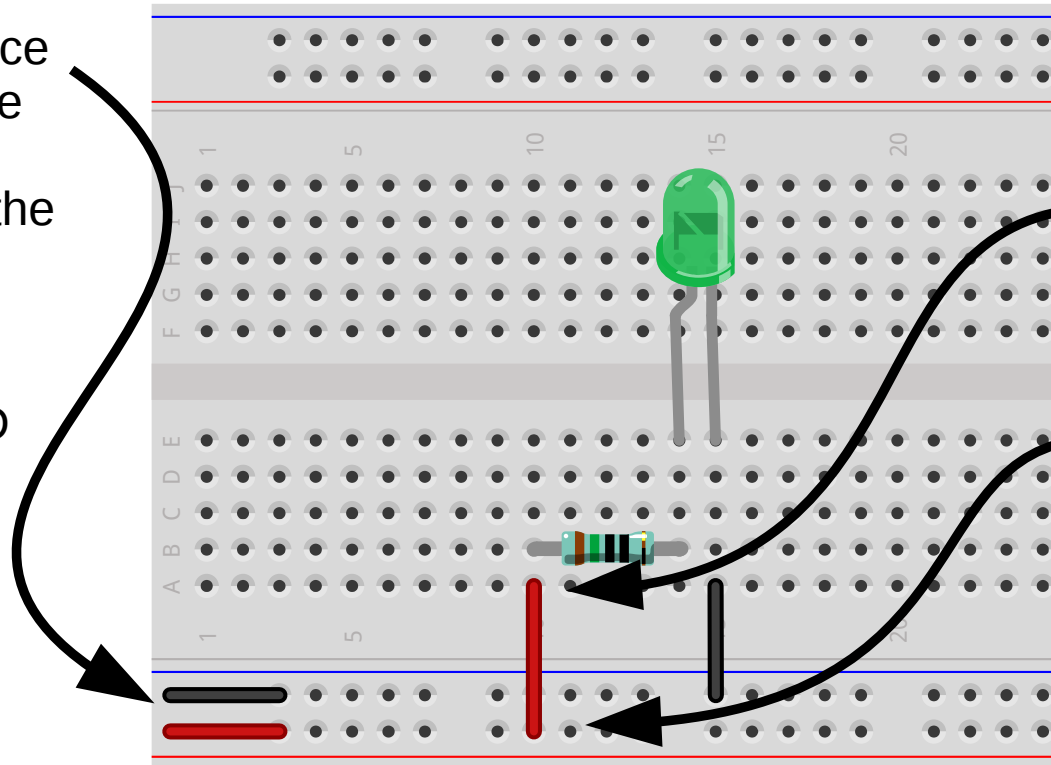

Wire:

Top end aligns vertically with resistor's left wire

Bottom end in the power rail that's nearer to you